
EEEE BJT configurations

01 September 2020 02:3

BJT TRANSISTOR CHARACTERISTICS

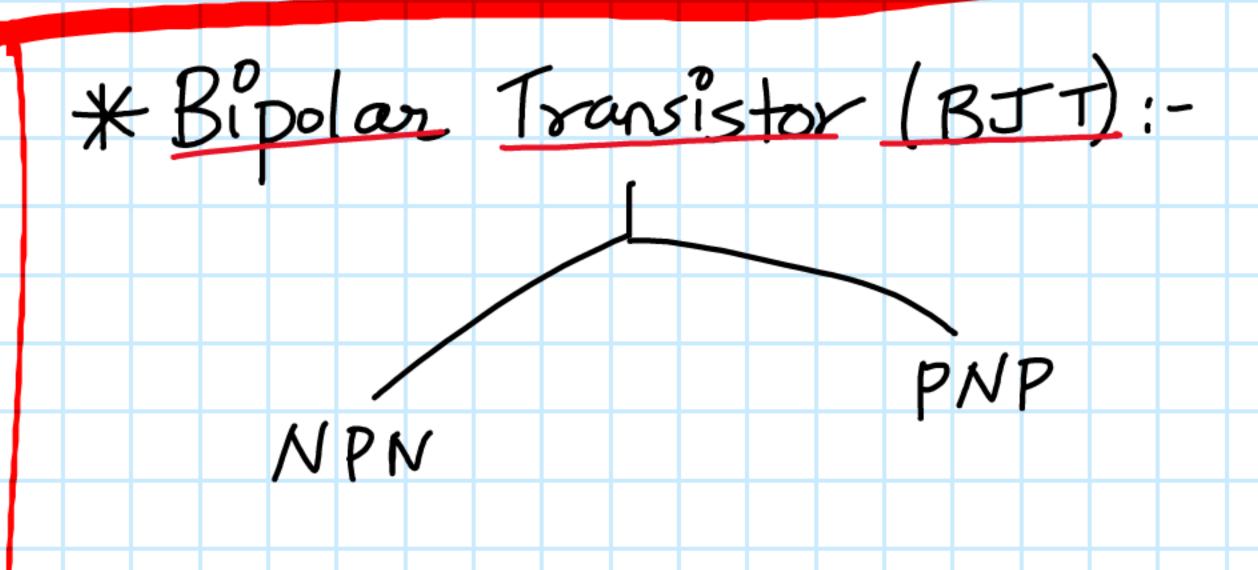

- * BIT Characteristics:-
 - 1 Input characteristics.

IP current Vs IIp voltage | olp voltage = constant

2) Outpot characteristics:

OP current V5 OP voltage | IP current = constant

- * Transistor configuration:-
 - The configuration's of the transistor

 are based on the connection of transistor

 terminal.
 - -> The three types of transistor circuit configuration are:-
 - () Common emittes
 - 2) Common Base
 - 3 Common Collector (Enritter follower)

