



PHASOR DIAGRAM OF TRANSFORMER

**Prepared By
ELECTRICALBABA.COM**

IMPORTANT POINTS FOR PHASOR OF TRANSFORMER


- Transformer when excited at no load, only takes excitation current which leads the working Flux by Hysteretic angle α .
- Excitation current is made up of two components, one in phase with the applied Voltage V is called Core Loss component (I_c) and another in phase with the working Flux Φ called Magnetizing Current (I_m).
- Electromotive Force (EMF) created by working Flux Φ lags behind it by 90 degree.
- When Transformer is connected with a Load, it takes extra current I' from the Source so that $N_1 I' = N_2 I_2$ where I' is called load component of Primary Current I

IMPORTANT POINTS FOR PHASOR OF TRANSFORMER

- So under load condition, I_1 = Primary Current, is phasor Sum of I' and Excitation Current I_e .



NO LOAD PHASOR OF A TRANSFORMER

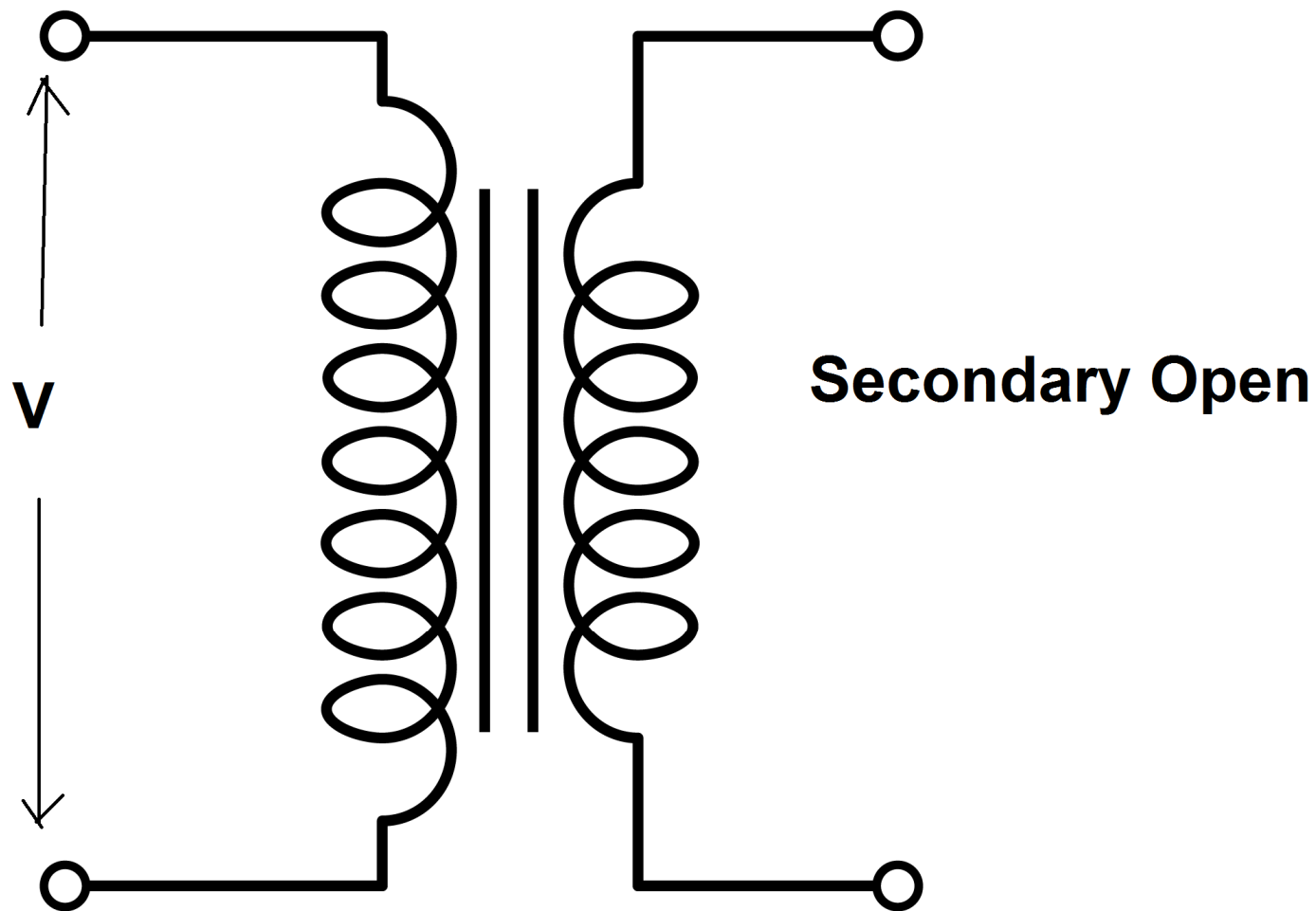


NO LOAD PHASOR OF A TRANSFORMER

- Working Flux Φ taken as Reference




NO LOAD PHASOR OF A TRANSFORMER

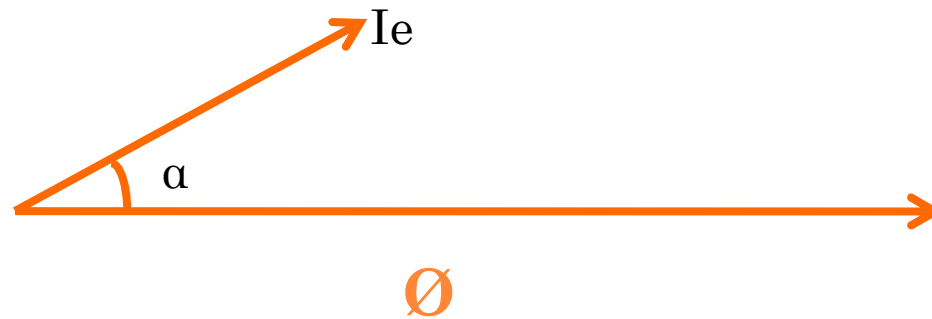- Excitation Current I_e leading \emptyset by α .




NO LOAD PHASOR OF A TRANSFORMER

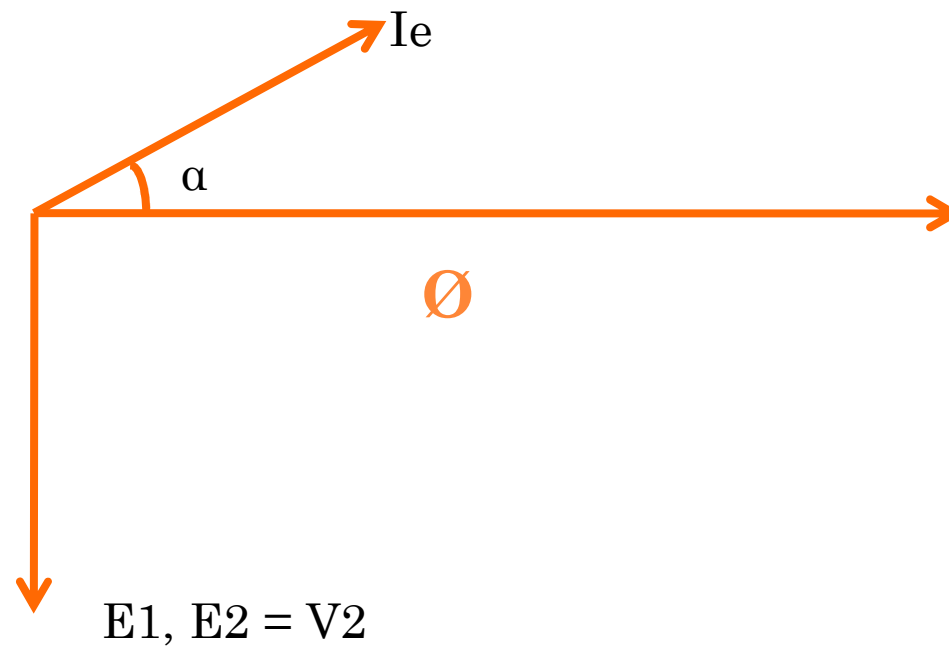- Induced EMF E_1 and E_2 lagging Flux by 90 degree.




NO LOAD PHASOR OF A TRANSFORMER

- $V_1' = -E_1$

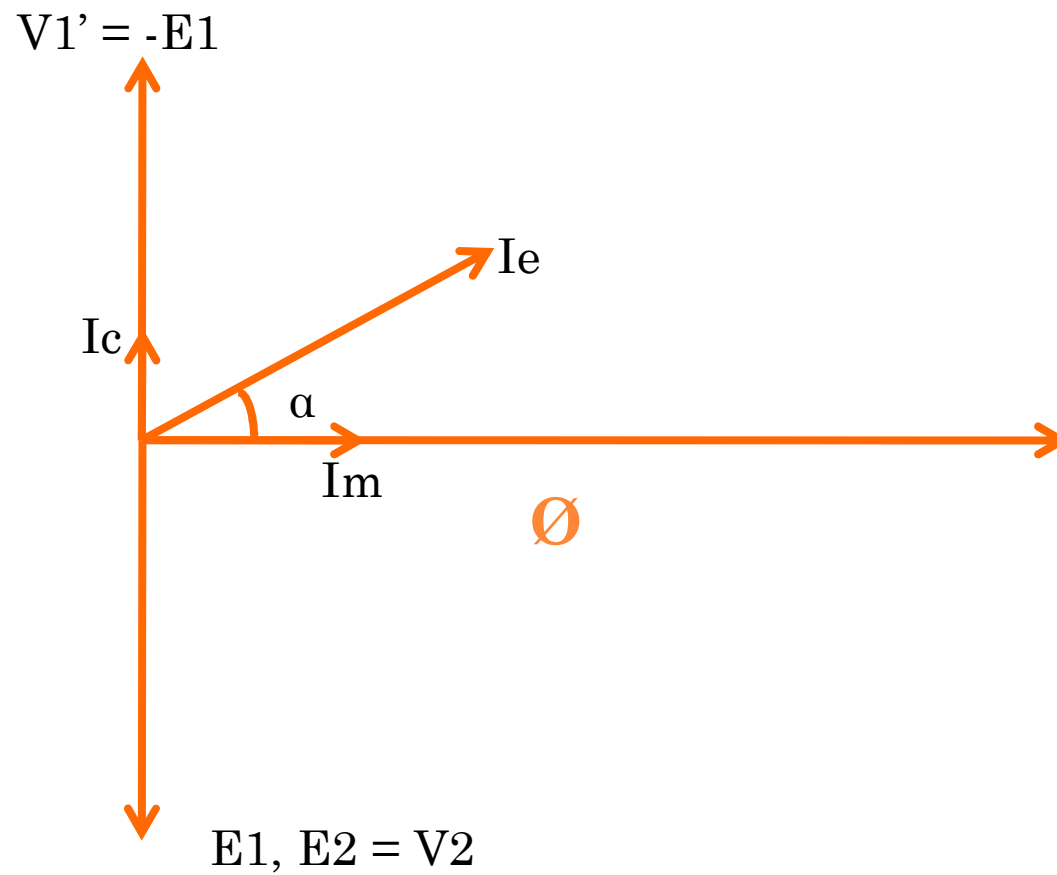


NO LOAD PHASOR OF A TRANSFORMER

- Voltage drop $r_1 I_e$ in Primary.

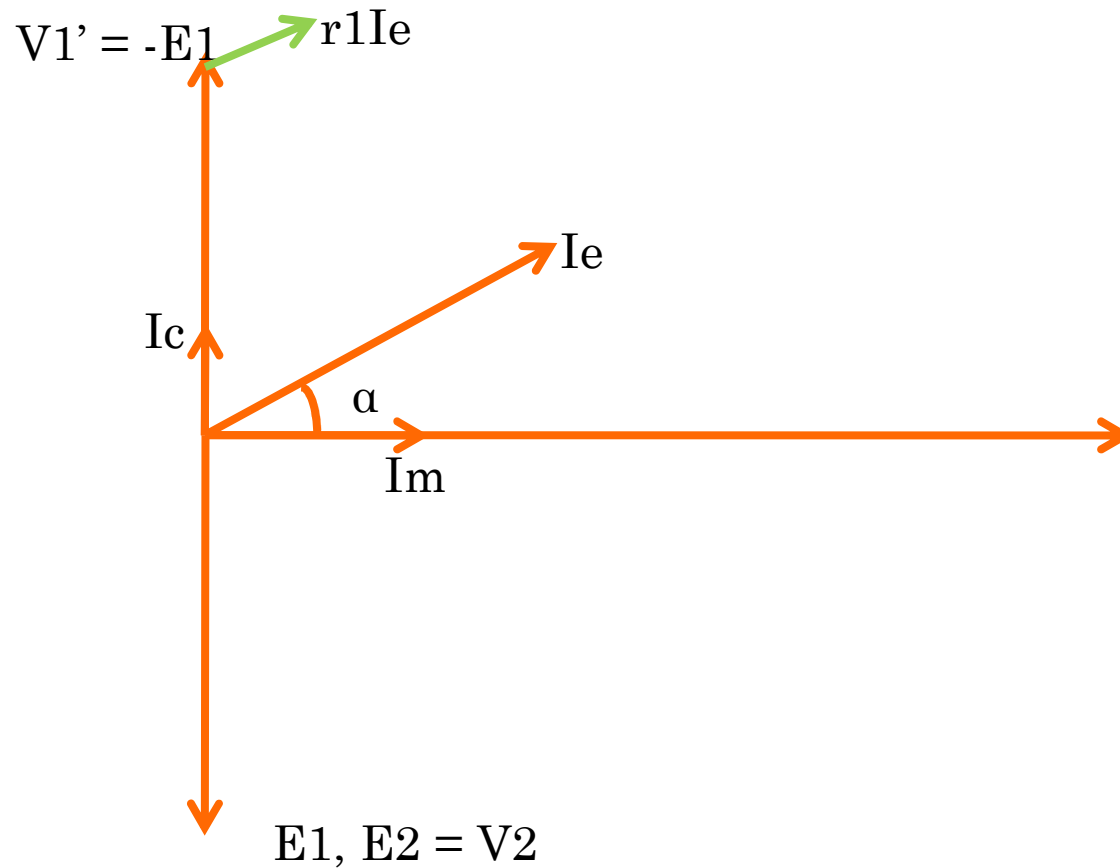


NO LOAD PHASOR OF A TRANSFORMER

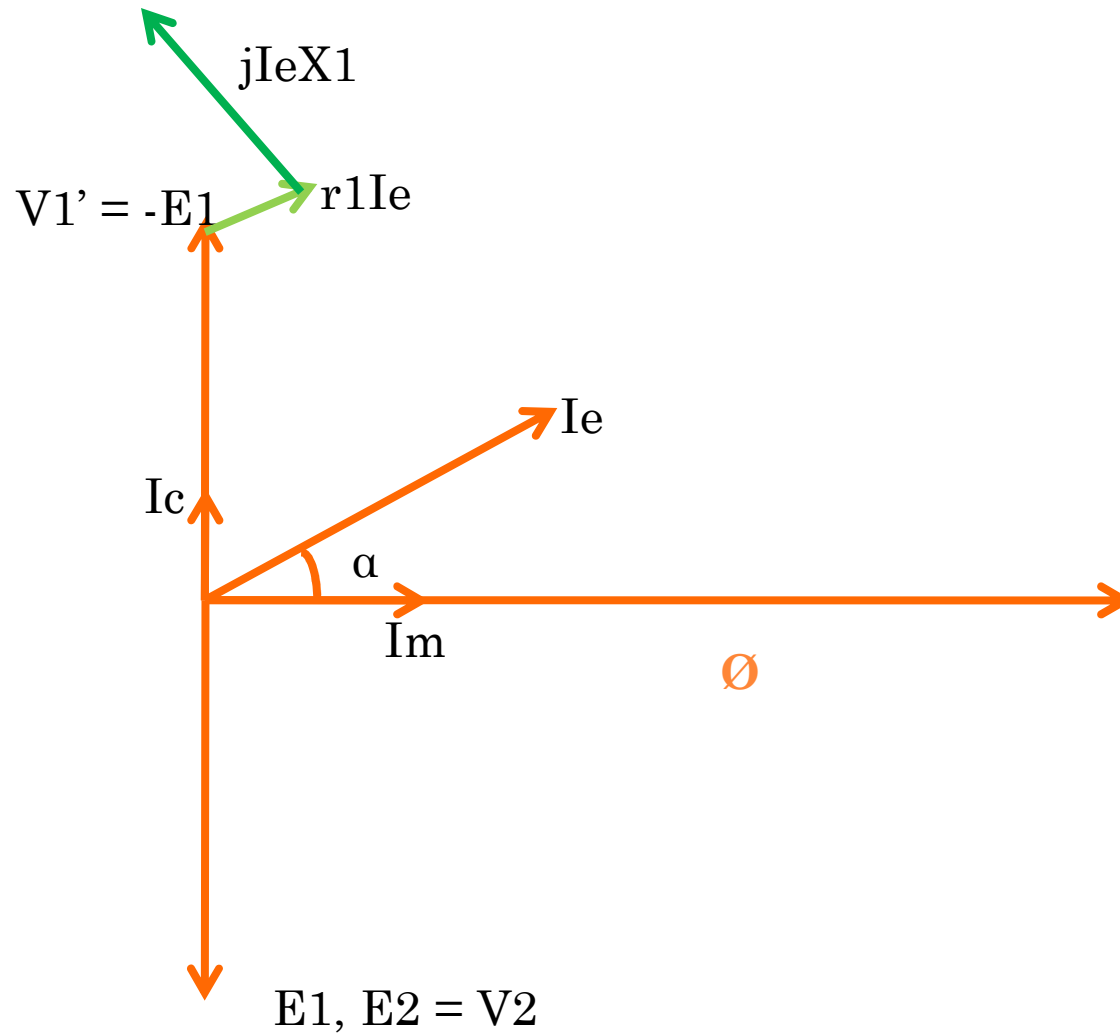Voltage drop $I_e X_1$ in Primary due to reactance.




NO LOAD PHASOR OF A TRANSFORMER

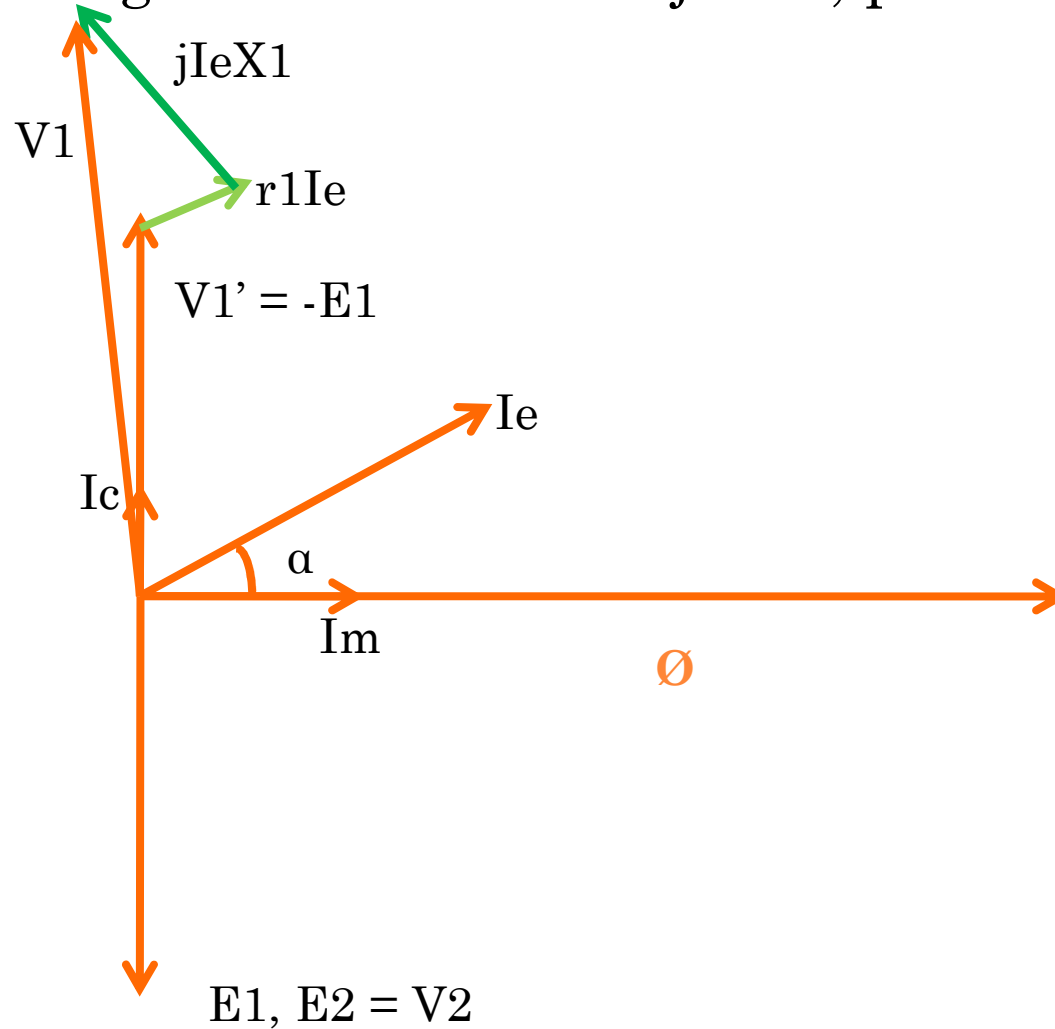Source Voltage $V_1 = V_1' + r_1 I_e + j I_e X_1$, phasor sum.




NO LOAD PHASOR OF A TRANSFORMER

No load Power Factor = $\cos\theta$

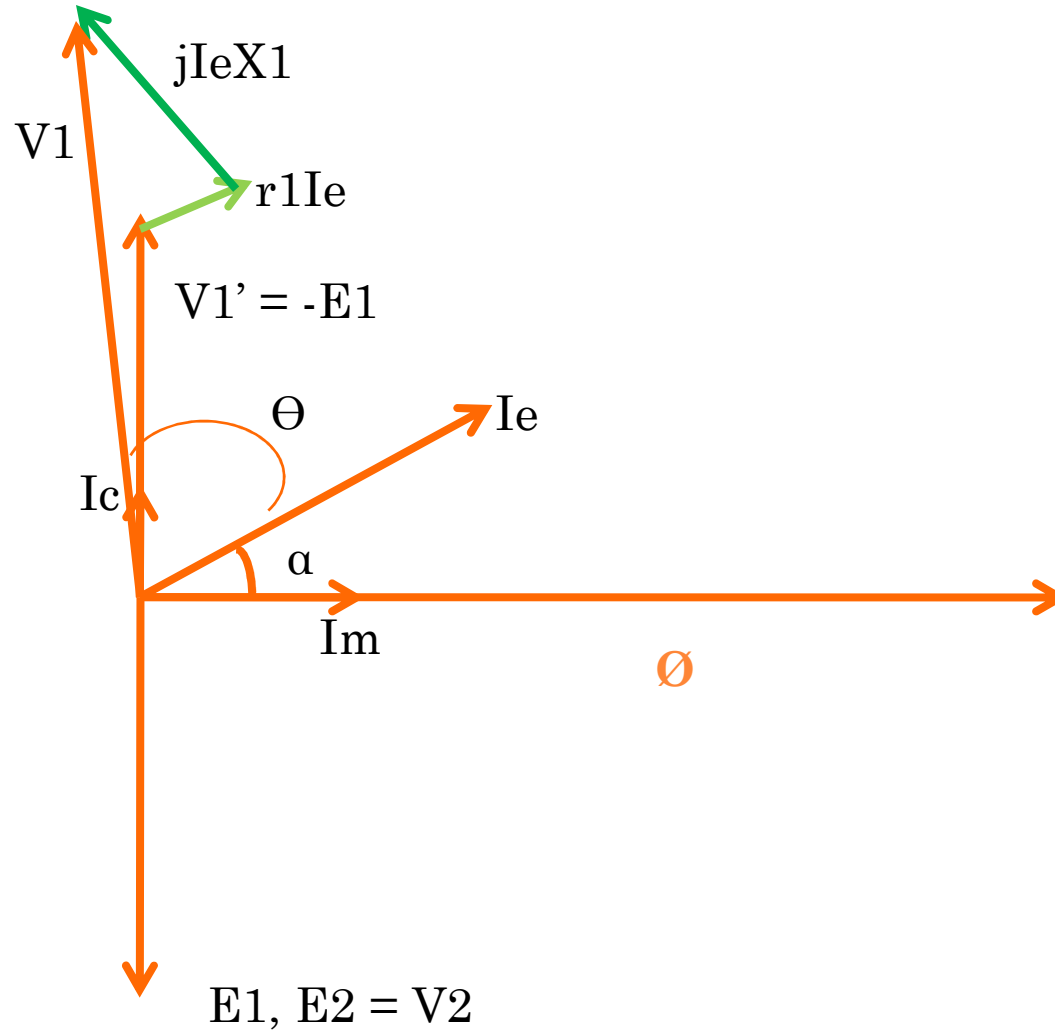

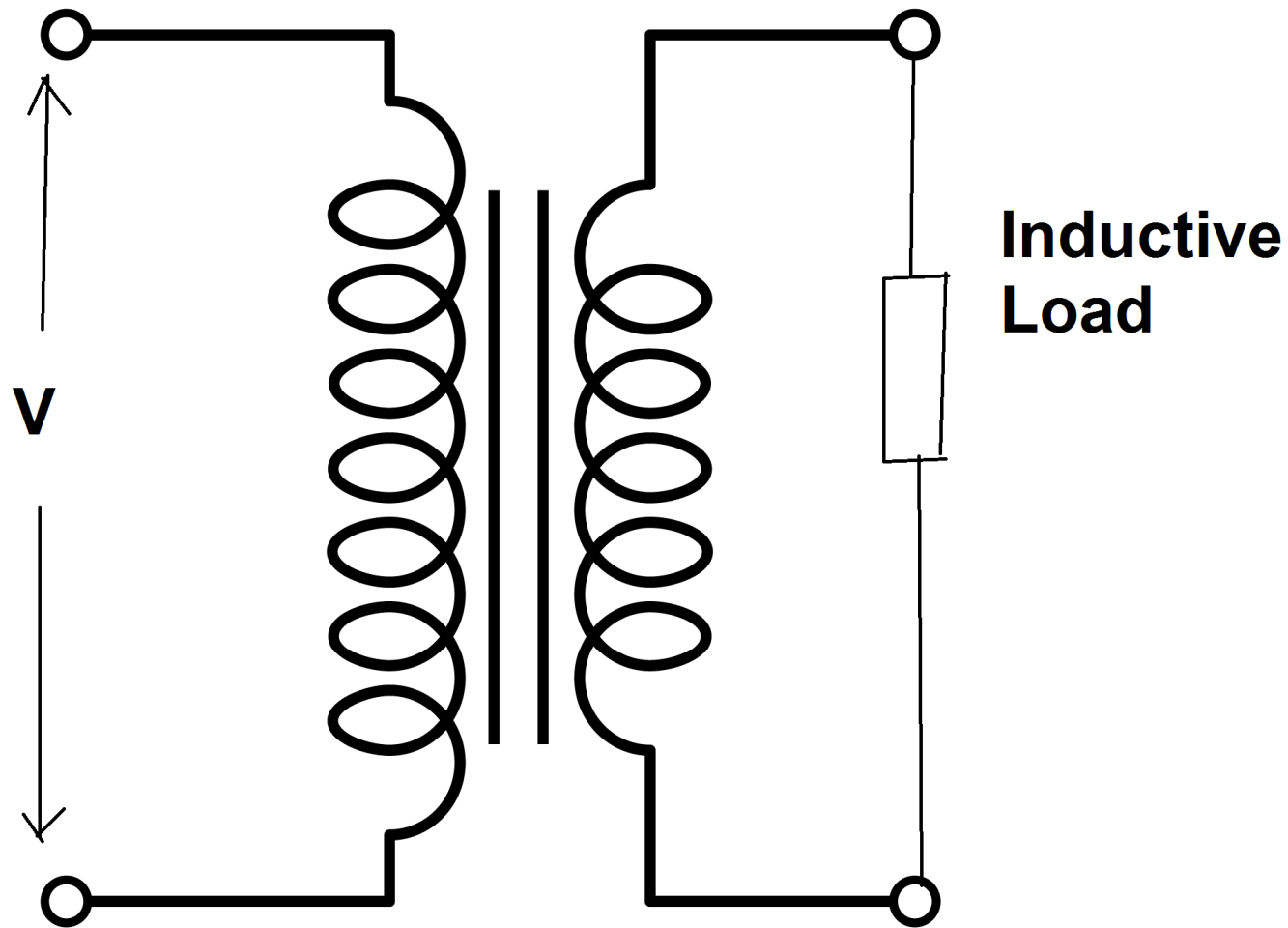PHASOR OF A TRANSFORMER FOR INDUCTIVE LOAD



PHASOR OF A TRANSFORMER FOR INDUCTIVE LOAD

- As load is inductive, secondary current will lag secondary load voltage V_2 by some angle.
- r_1 = Primary winding Resistance
- X_1 = Primary winding leakage Reactance
- r_2 = Secondary winding Resistance
- X_2 = Secondary winding leakage Reactance



PHASOR OF A TRANSFORMER FOR INDUCTIVE LOAD


- Working Flux Φ is taken as reference.




PHASOR OF A TRANSFORMER FOR INDUCTIVE LOAD



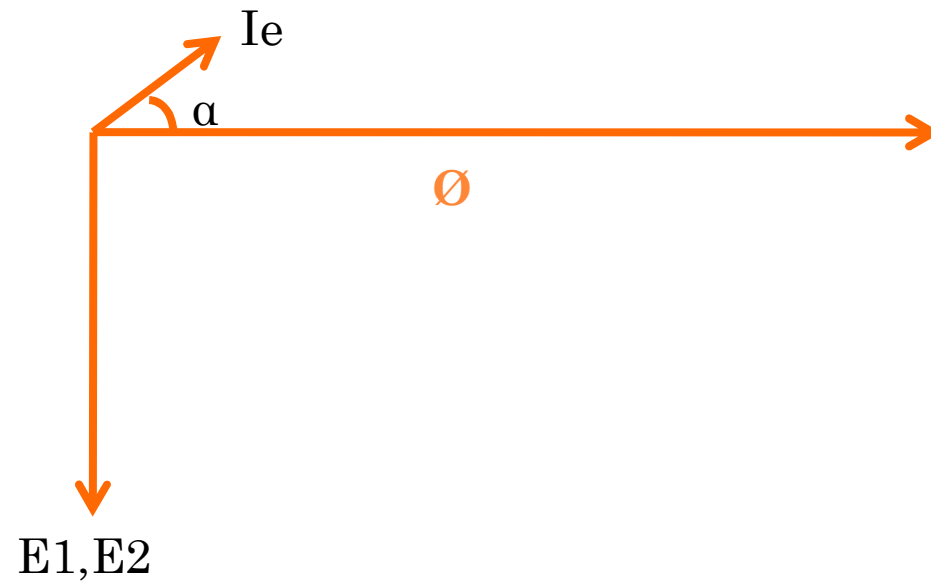
PHASOR OF A TRANSFORMER FOR INDUCTIVE LOAD



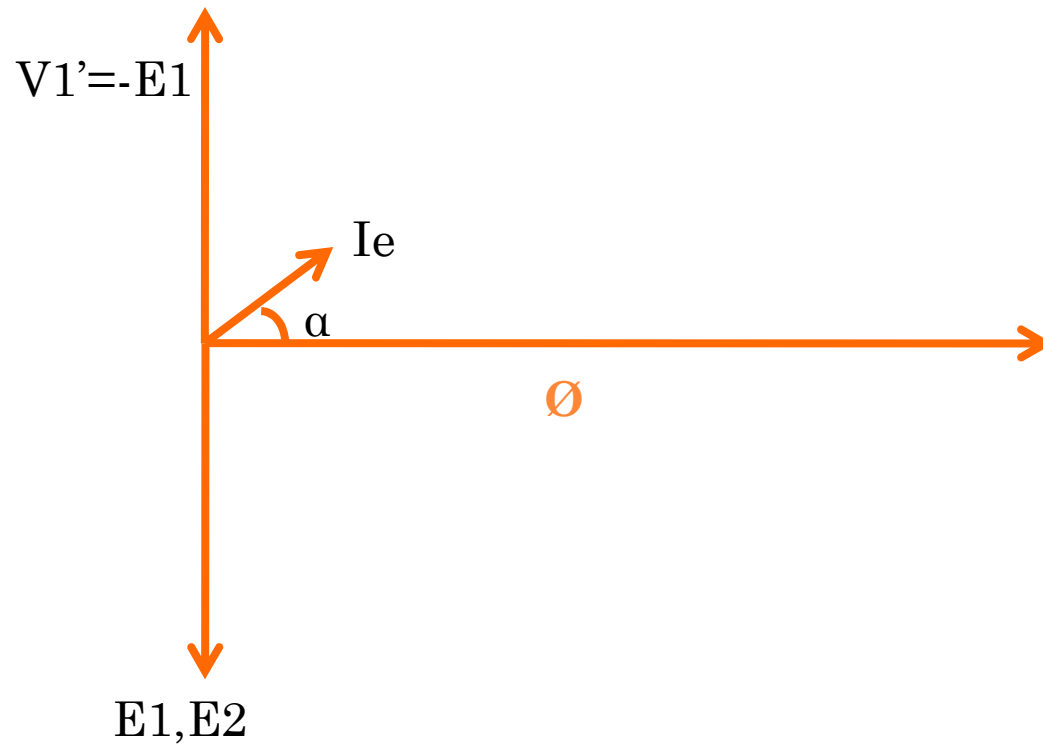PHASOR OF A TRANSFORMER FOR INDUCTIVE LOAD




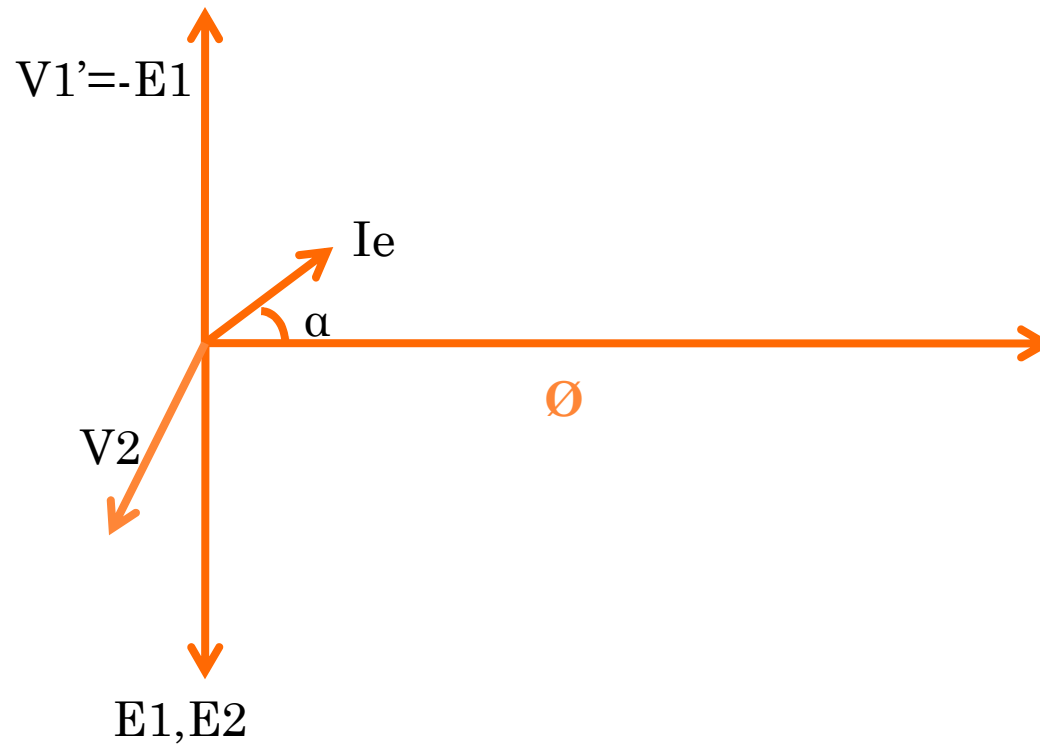PHASOR OF A TRANSFORMER FOR INDUCTIVE LOAD




PHASOR OF A TRANSFORMER FOR INDUCTIVE LOAD

- Working Flux Φ is taken as reference.

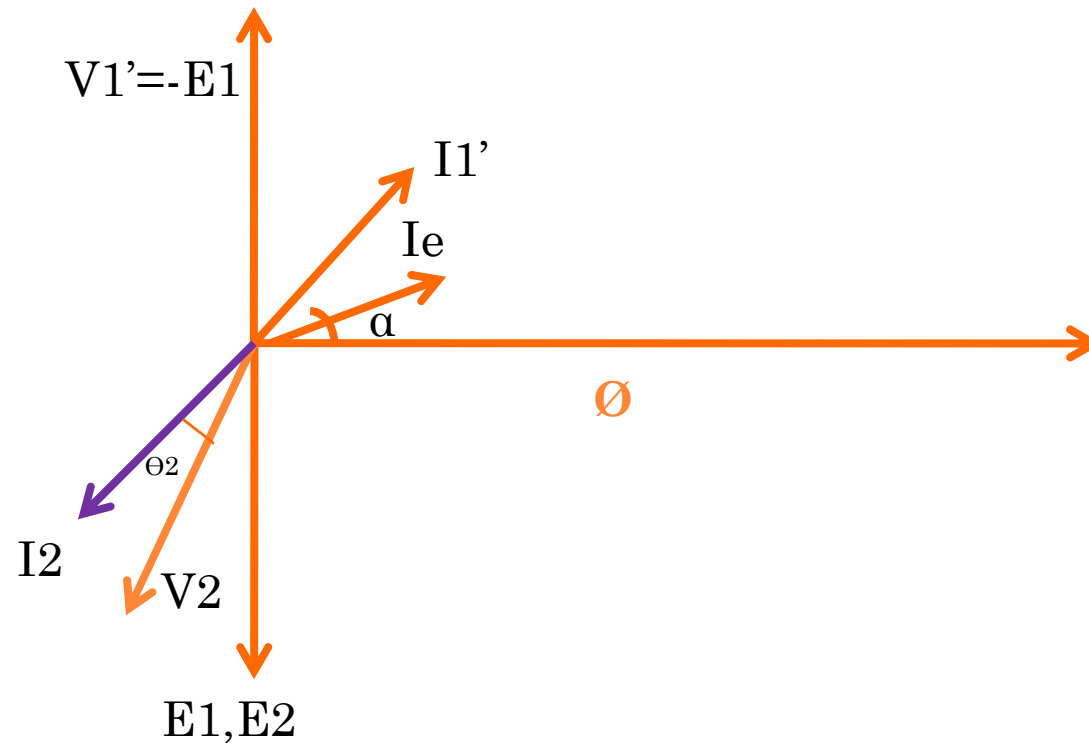


PHASOR OF A TRANSFORMER FOR INDUCTIVE LOAD

- Working Flux Φ is taken as reference.

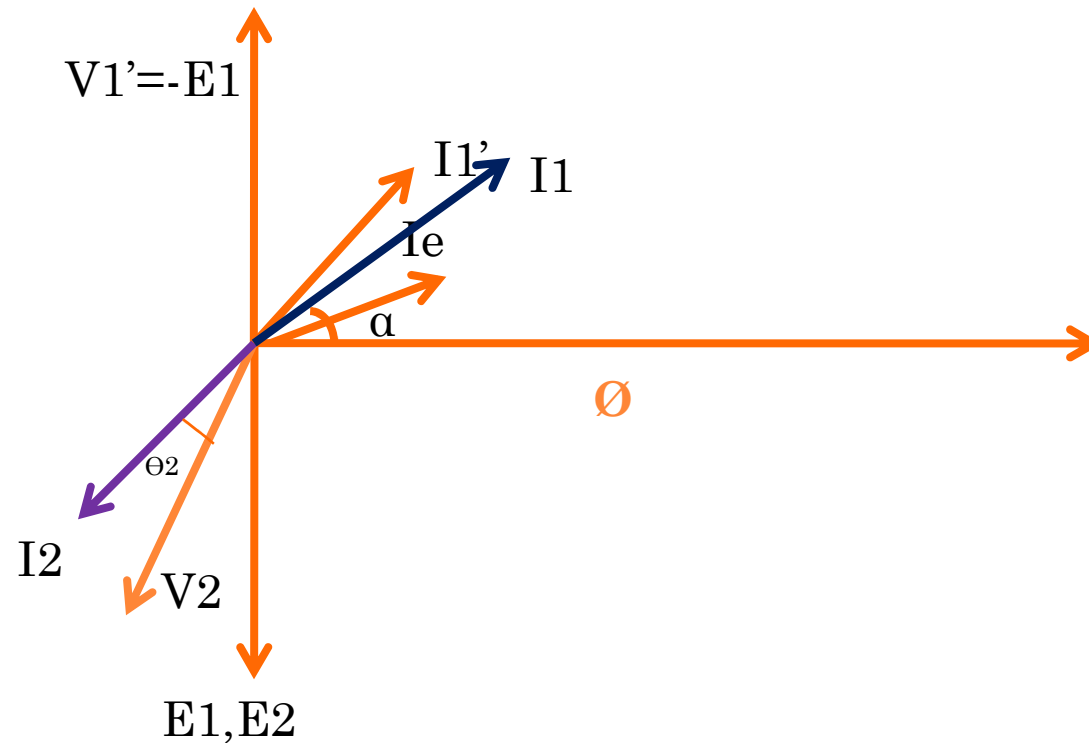


PHASOR OF A TRANSFORMER FOR INDUCTIVE LOAD

- Working Flux Φ is taken as reference.

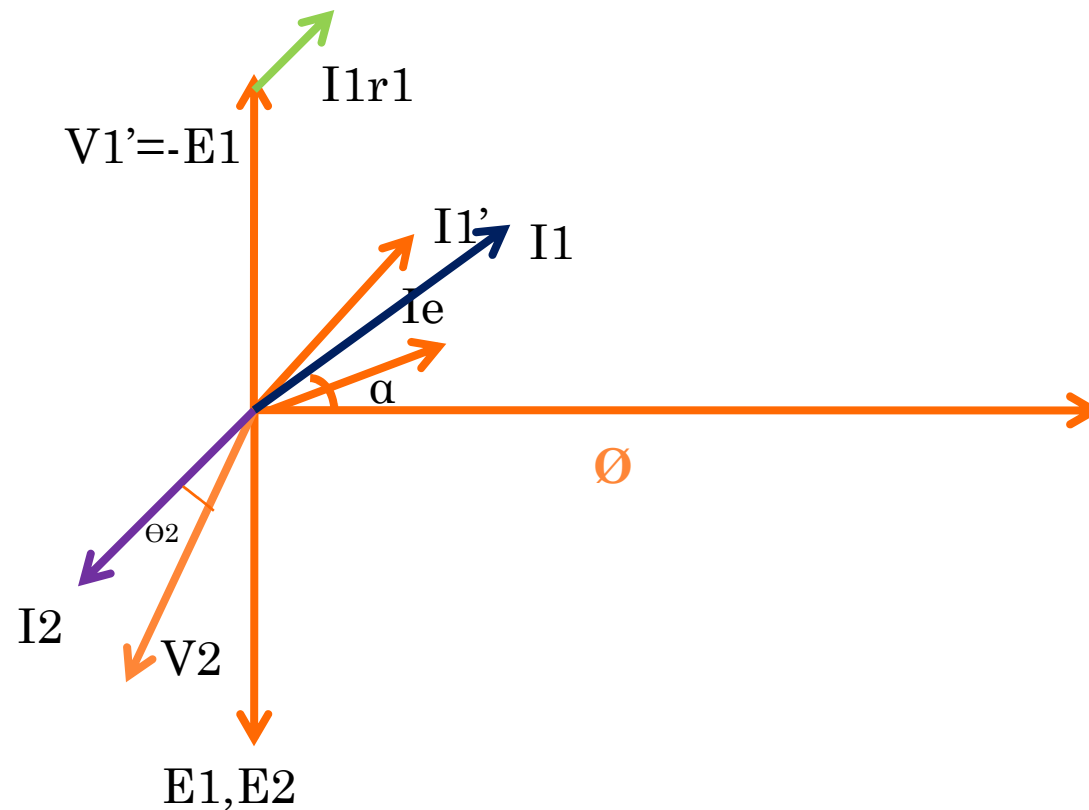


PHASOR OF A TRANSFORMER FOR INDUCTIVE LOAD

- Working Flux Φ is taken as reference.

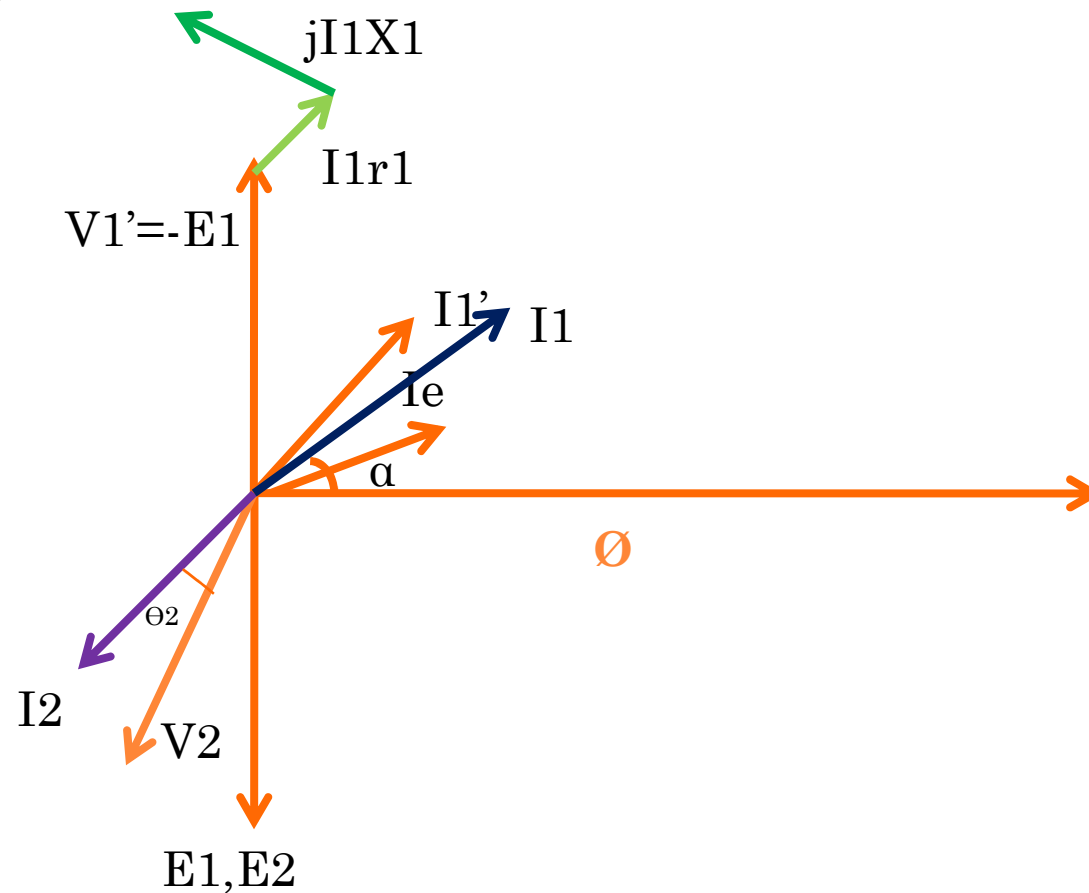


PHASOR OF A TRANSFORMER FOR INDUCTIVE LOAD

- Working Flux Φ is taken as reference.

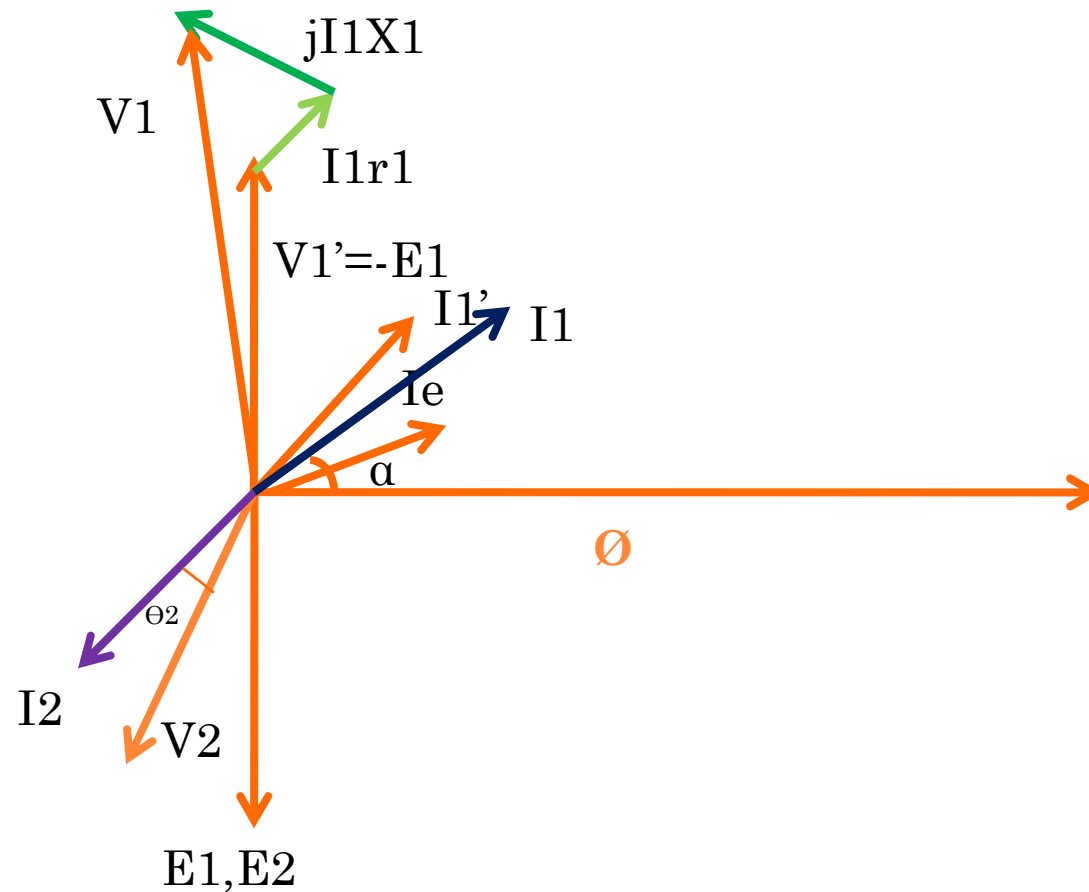


PHASOR OF A TRANSFORMER FOR INDUCTIVE LOAD


- Working Flux Φ is taken as reference.

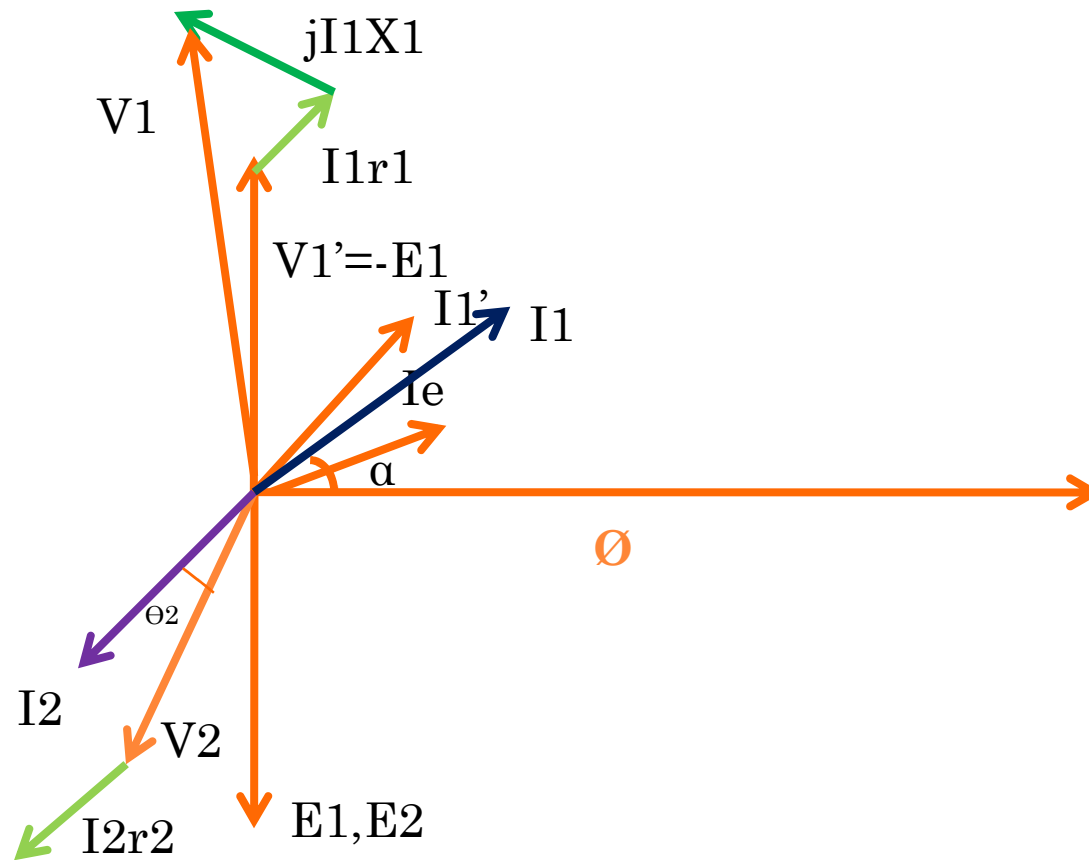

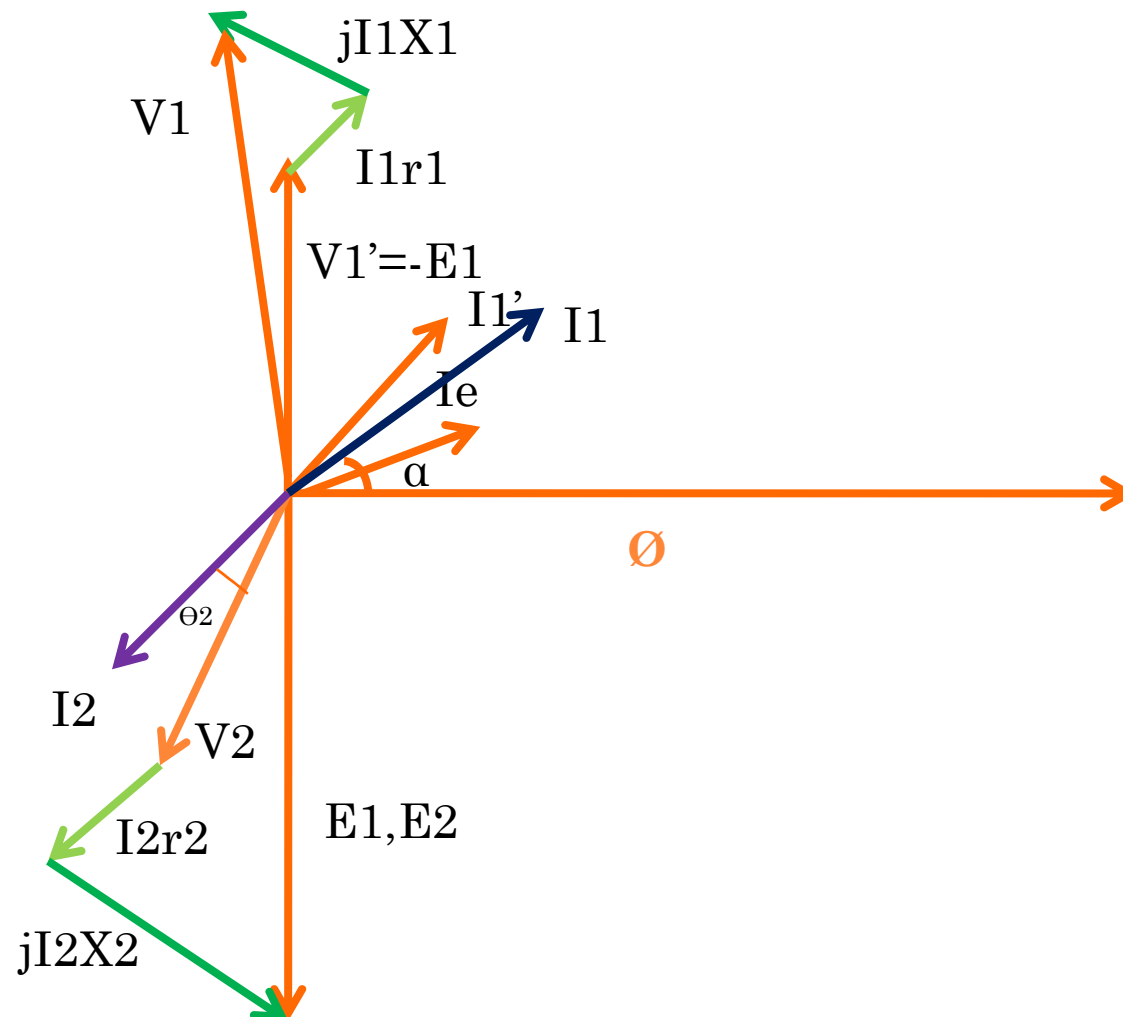- $E_2 = V_2 + I_2 r_2 + j I_2 X_2$, phasor sum




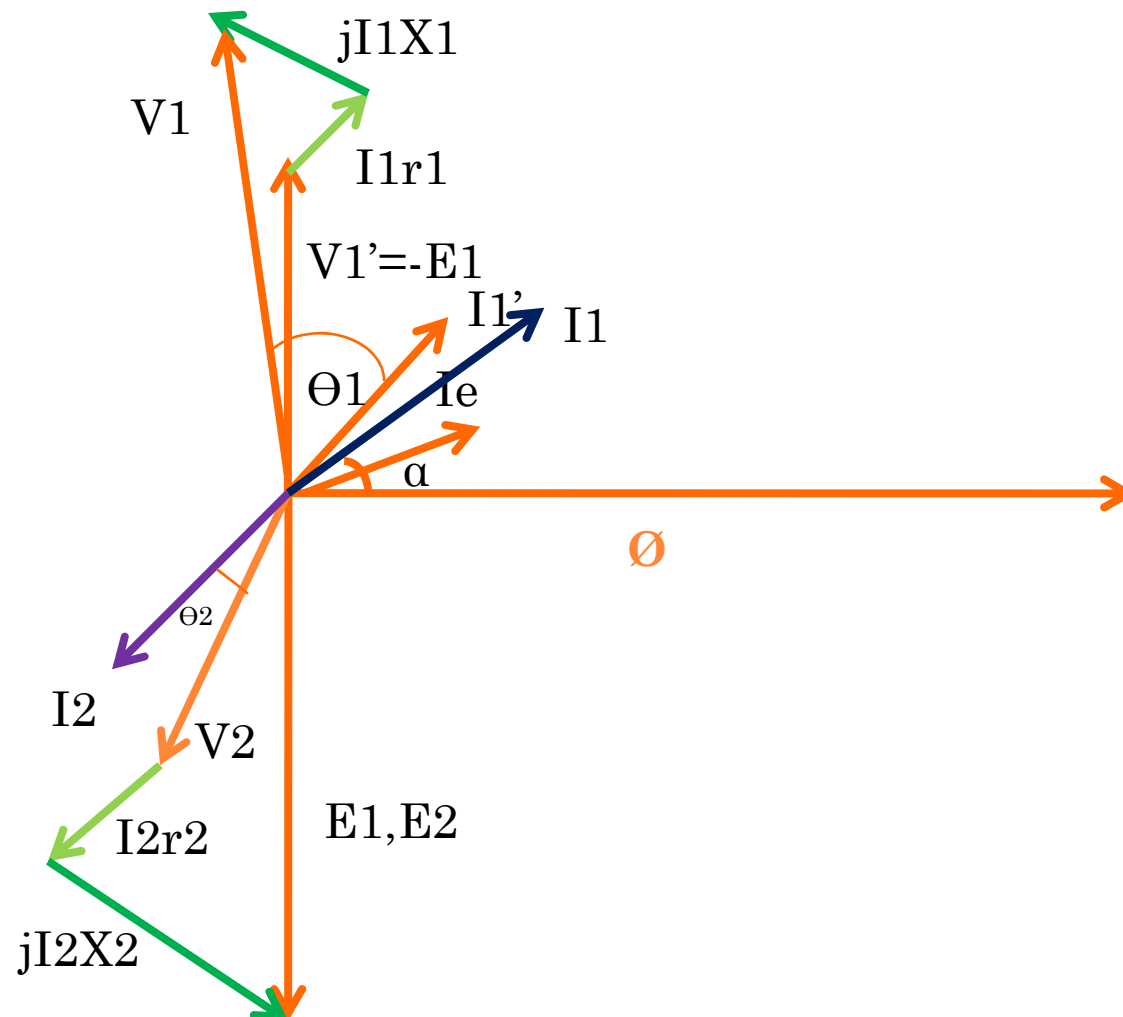- Primary Power Factor = $\cos \theta_1$, angle between V_1 & I_1 .



PHASOR OF A TRANSFORMER FOR CAPACITIVE LOAD

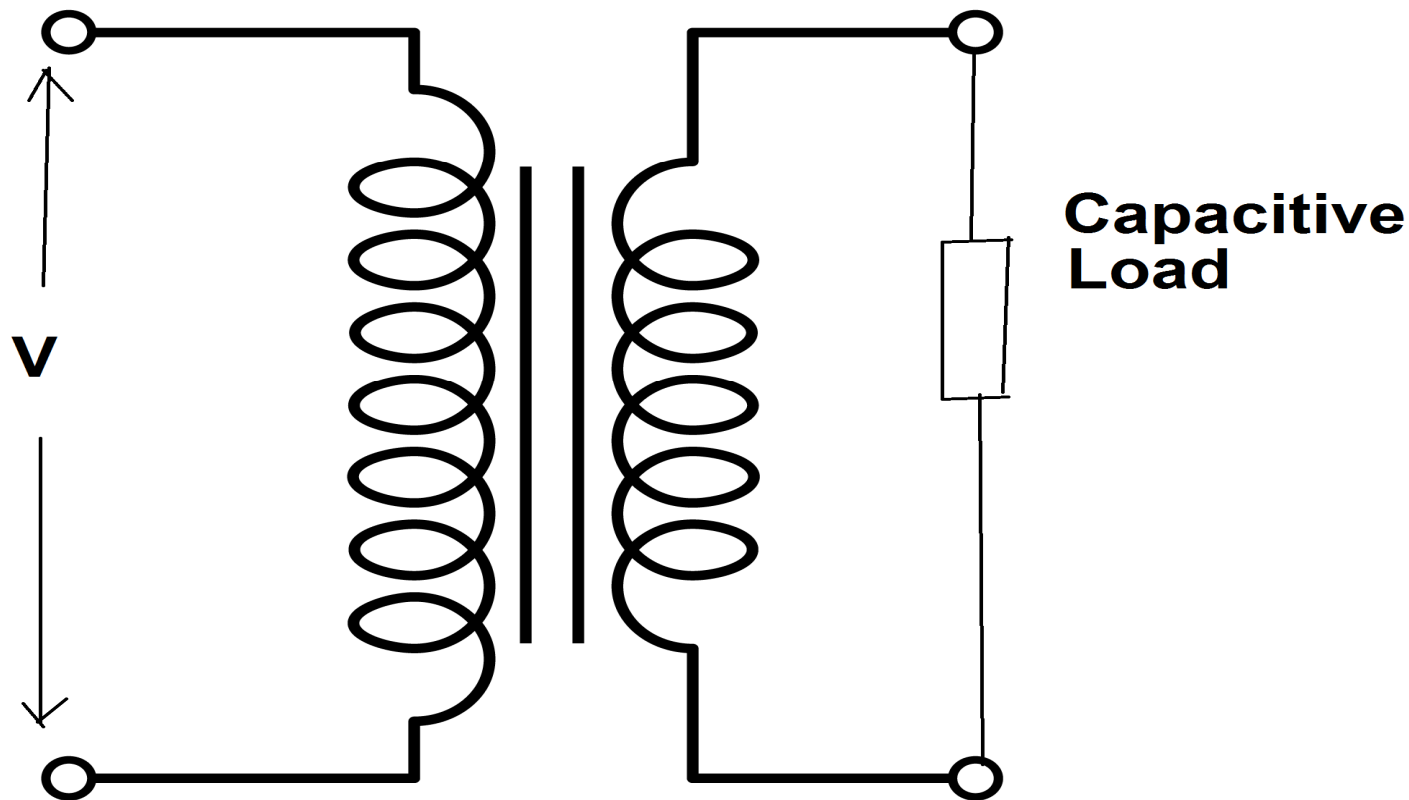- As load is capacitive, secondary current will lead secondary load voltage V_2 by some angle.



PHASOR OF A TRANSFORMER FOR CAPACITIVE LOAD


- Working Flux Φ is taken as reference.




PHASOR OF A TRANSFORMER FOR CAPACITIVE LOAD



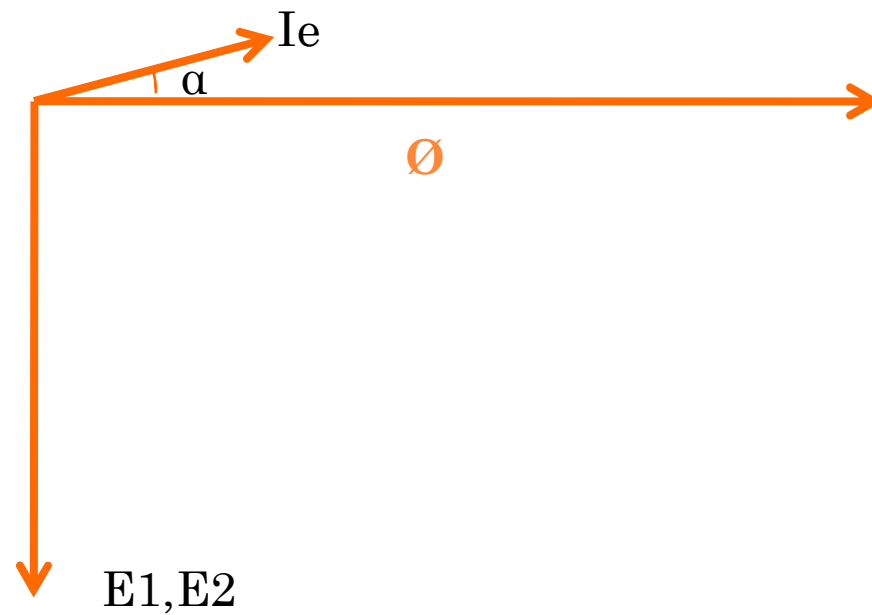
PHASOR OF A TRANSFORMER FOR CAPACITIVE LOAD



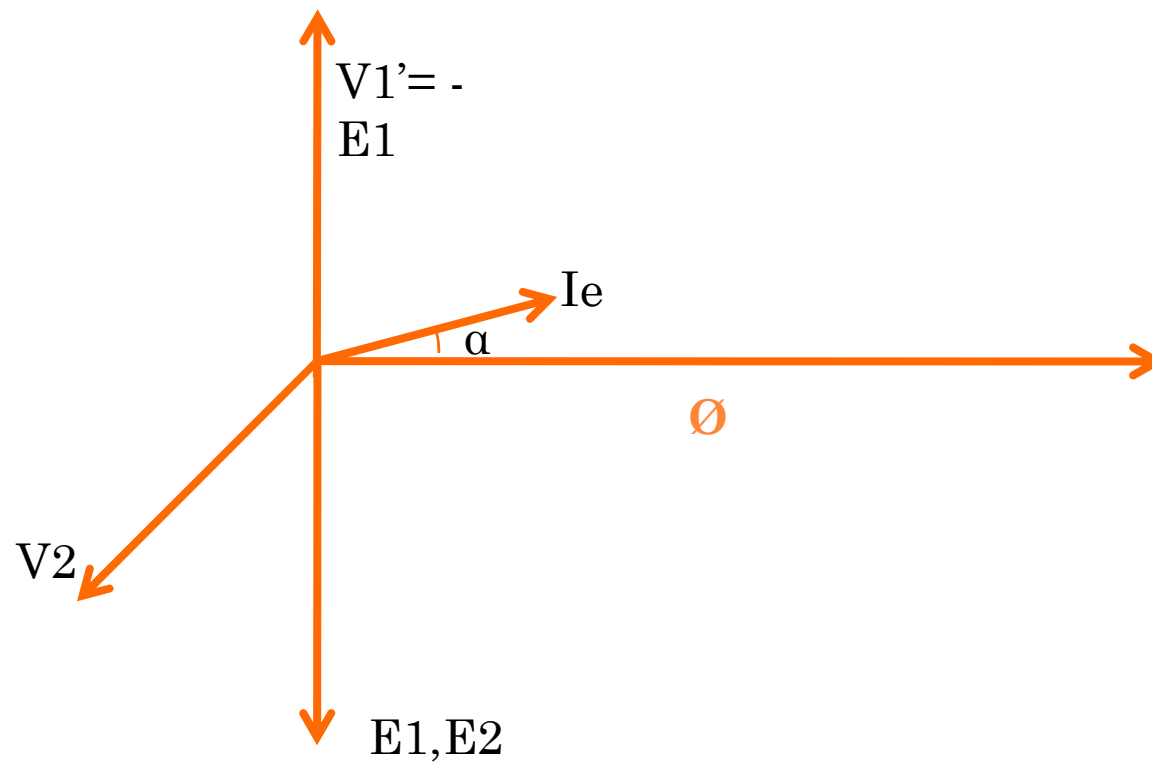
PHASOR OF A TRANSFORMER FOR CAPACITIVE LOAD



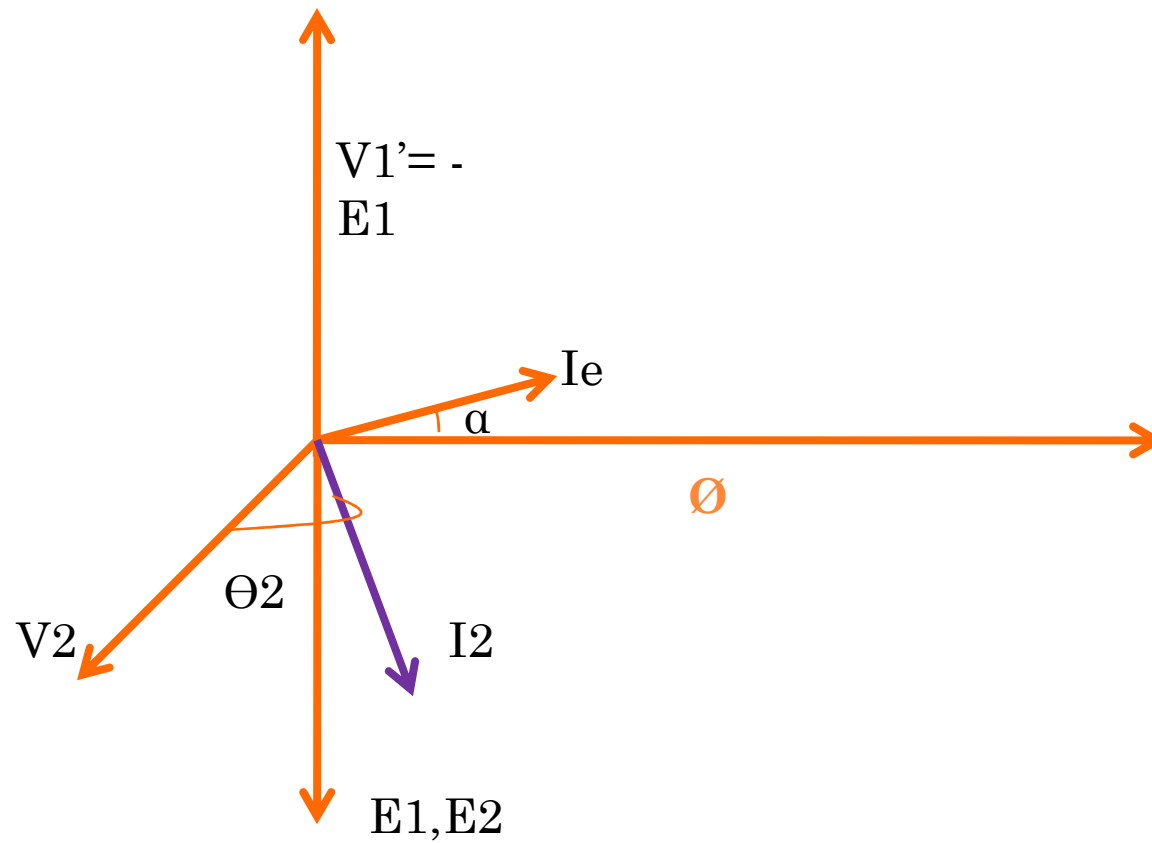
PHASOR OF A TRANSFORMER FOR CAPACITIVE LOAD



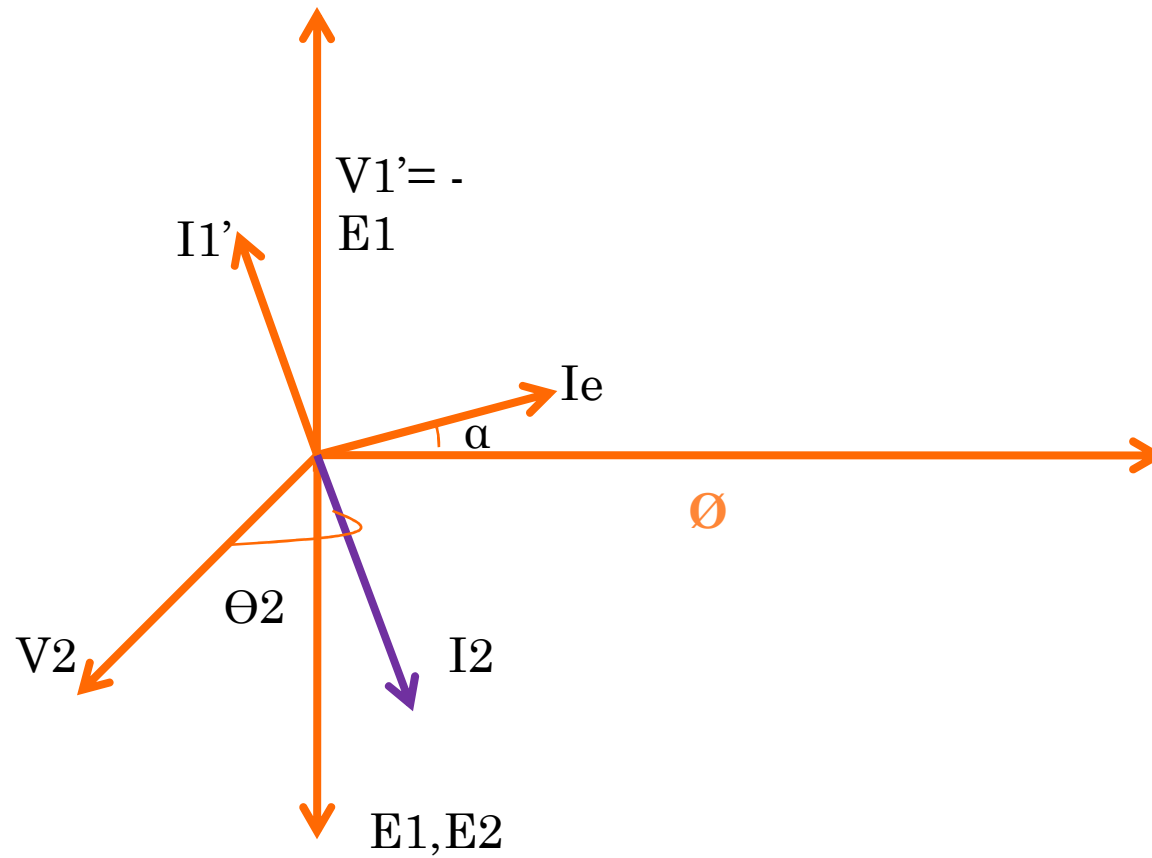
PHASOR OF A TRANSFORMER FOR CAPACITIVE LOAD



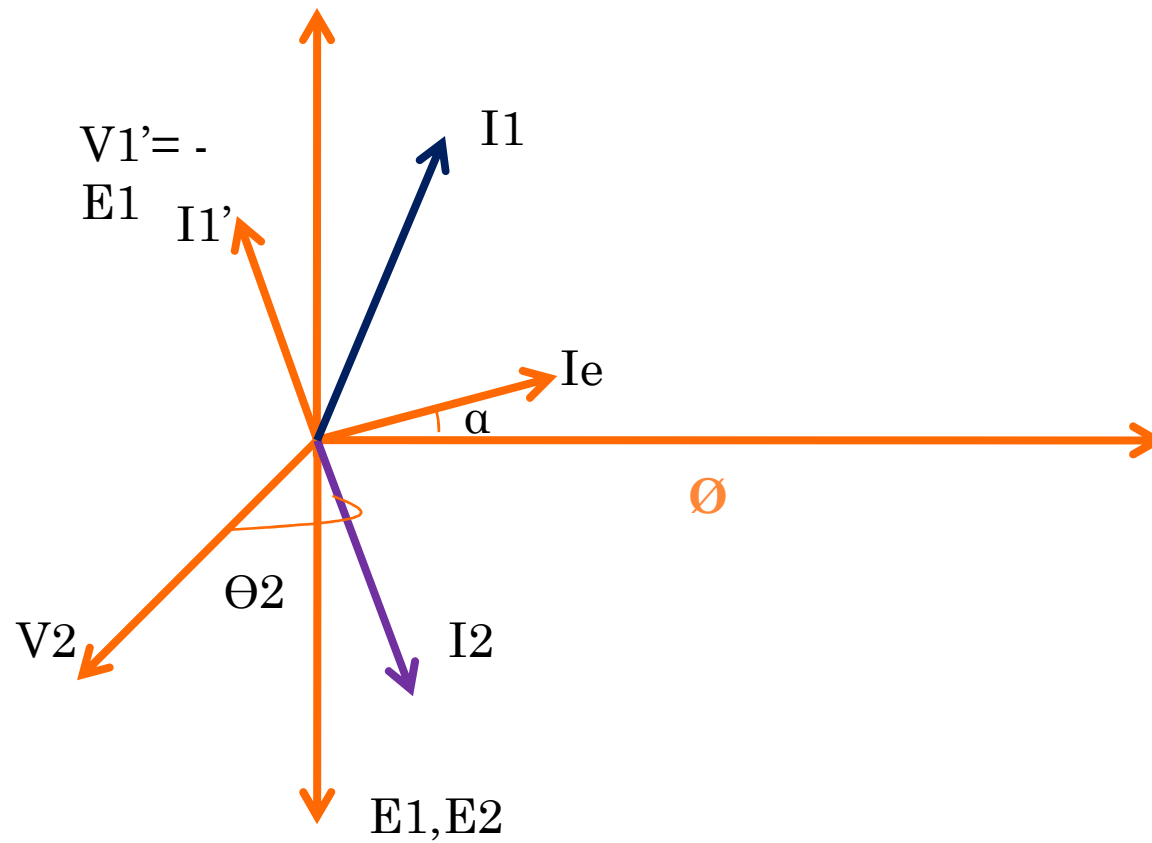
PHASOR OF A TRANSFORMER FOR CAPACITIVE LOAD



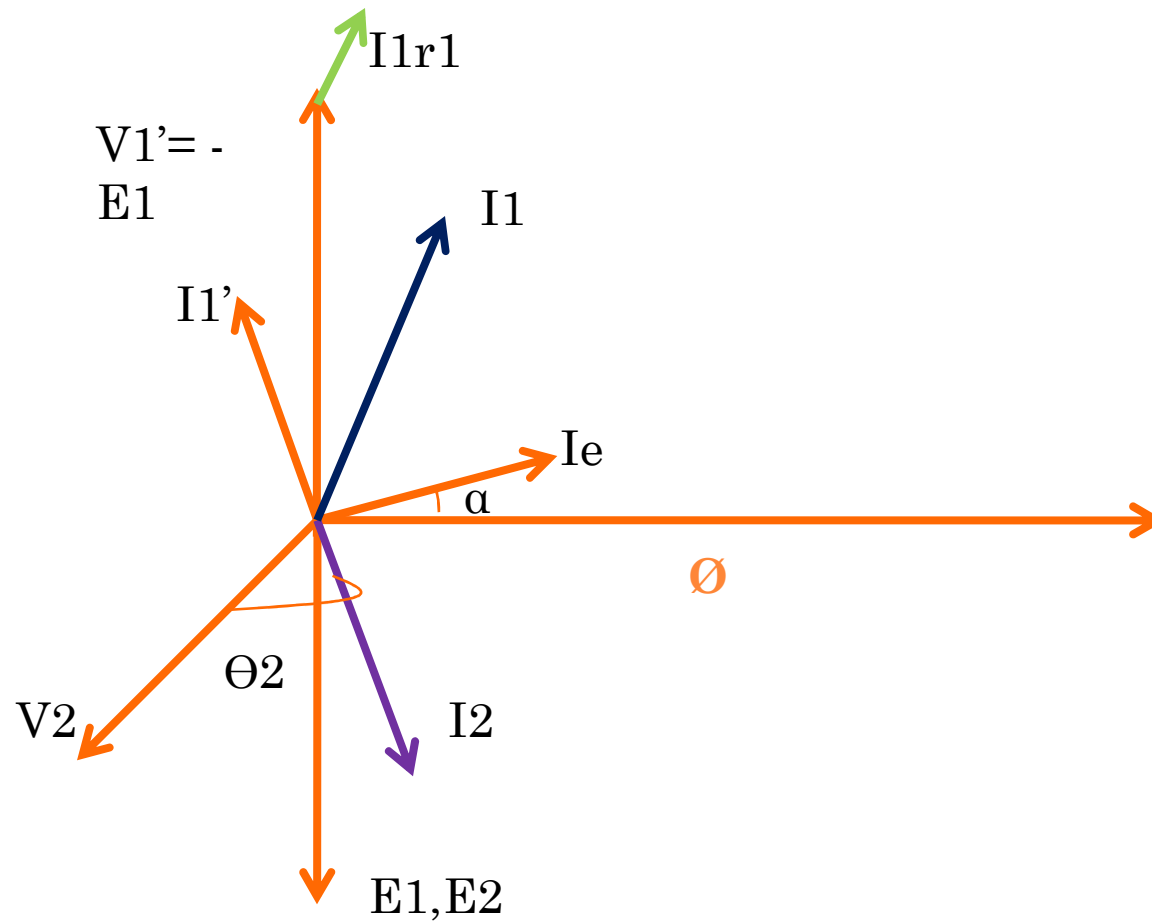
PHASOR OF A TRANSFORMER FOR CAPACITIVE LOAD



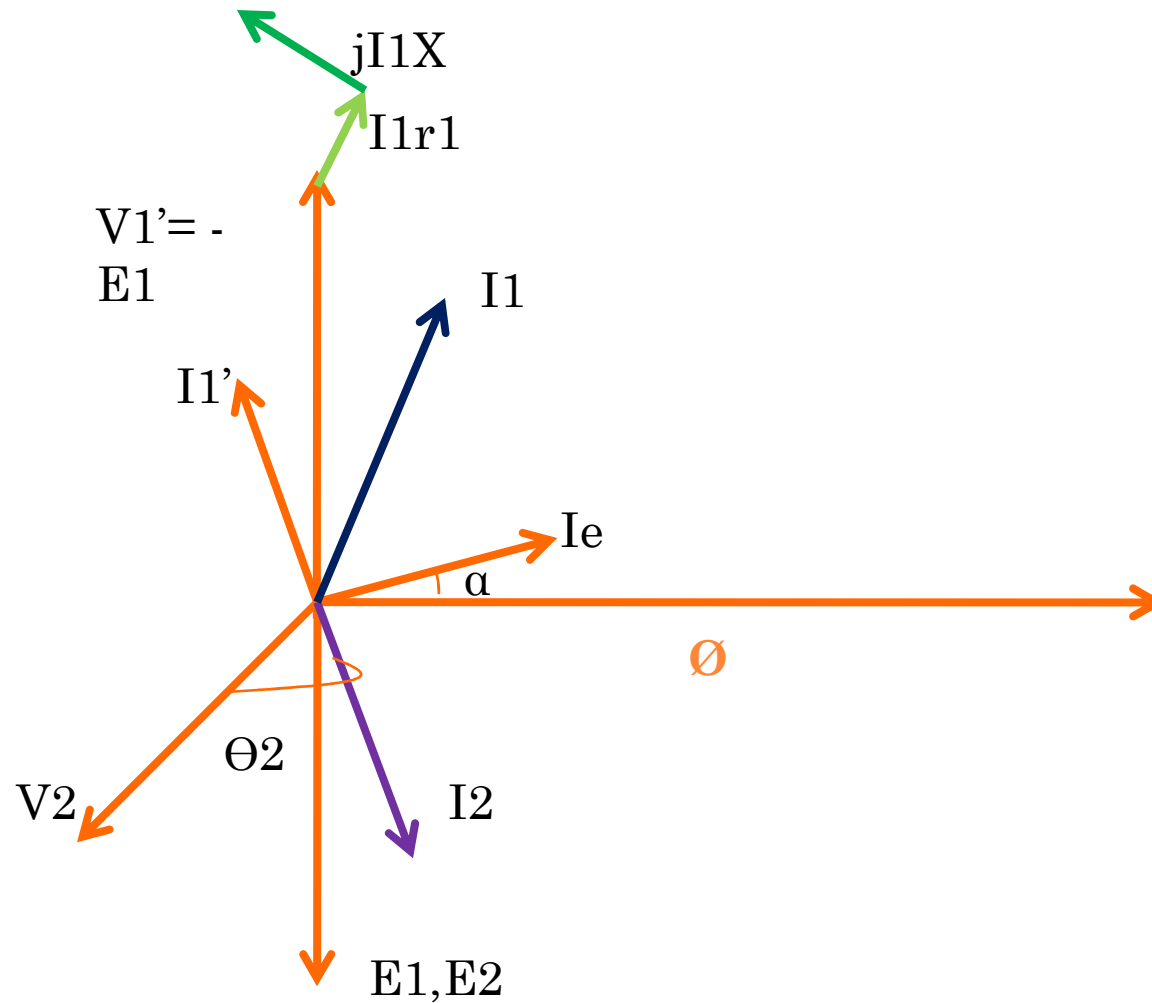
PHASOR OF A TRANSFORMER FOR CAPACITIVE LOAD



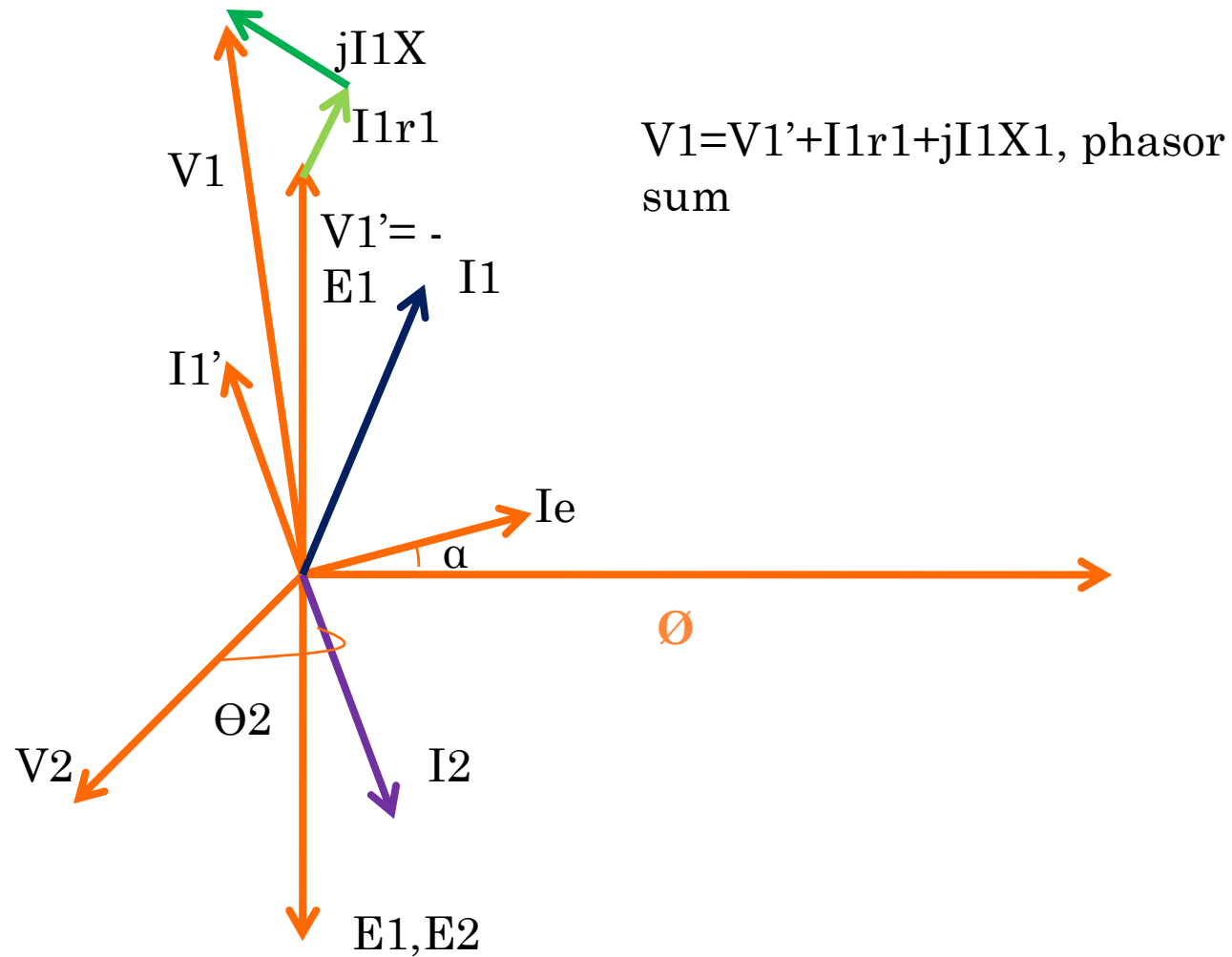
PHASOR OF A TRANSFORMER FOR CAPACITIVE LOAD



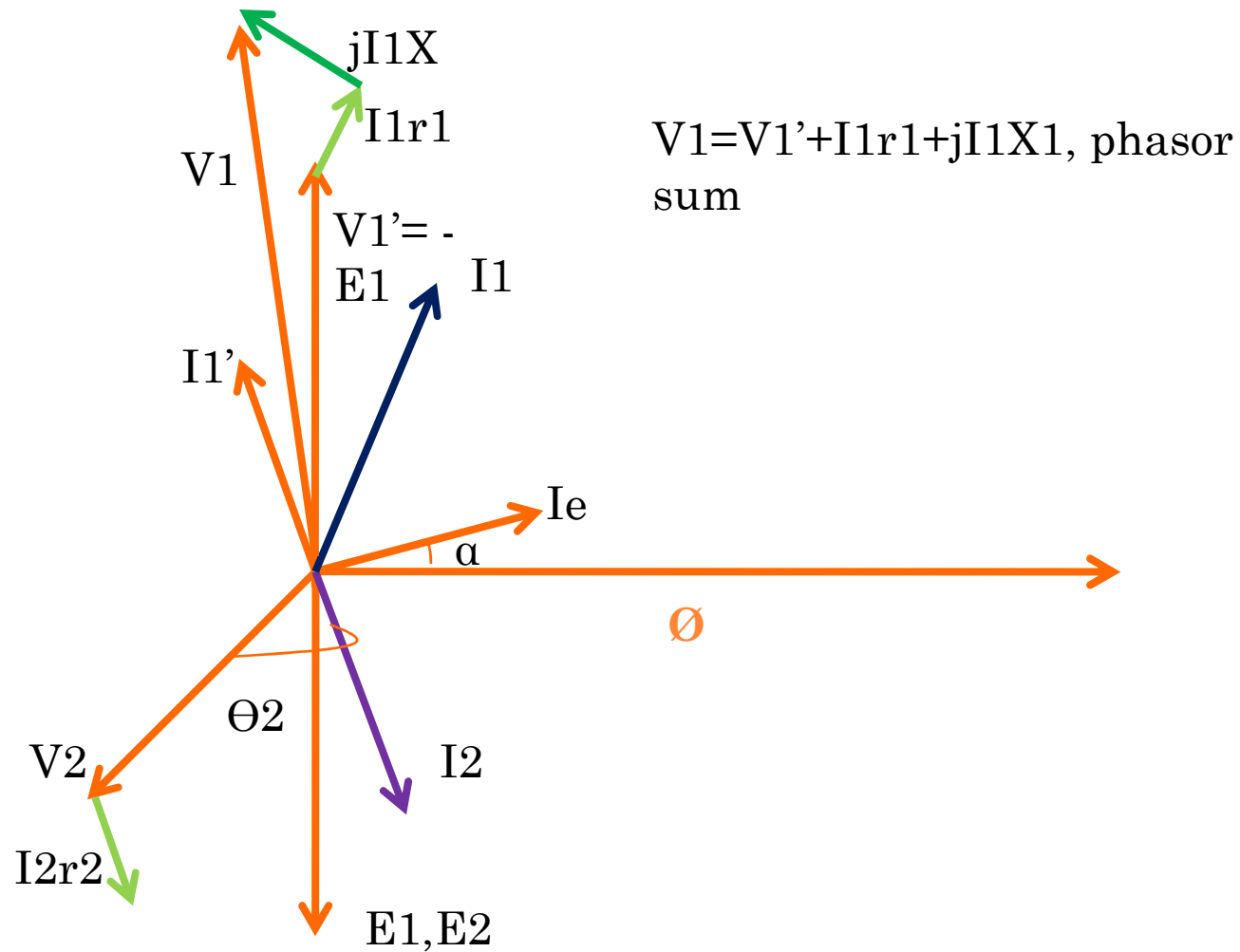
PHASOR OF A TRANSFORMER FOR CAPACITIVE LOAD



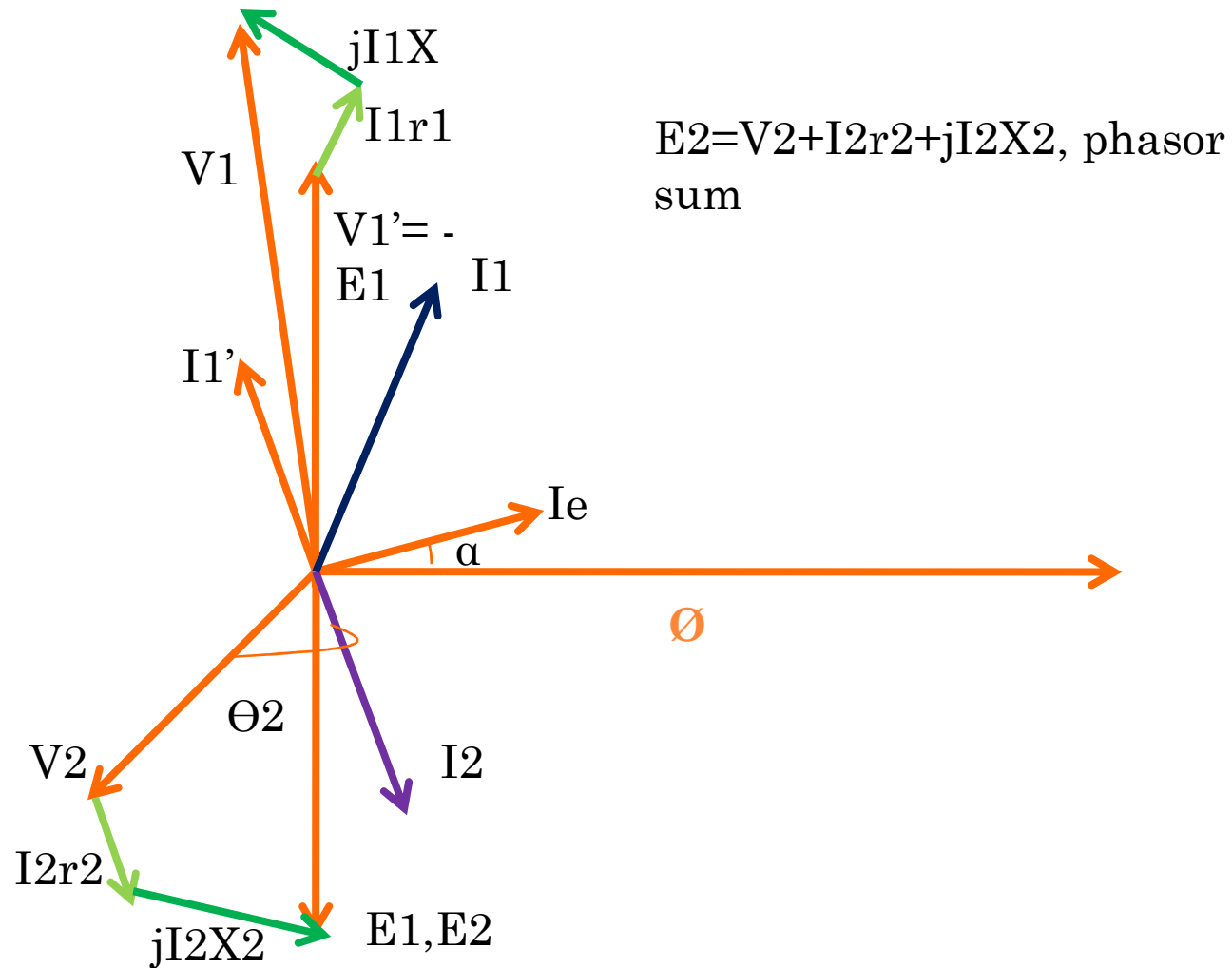
PHASOR OF A TRANSFORMER FOR CAPACITIVE LOAD



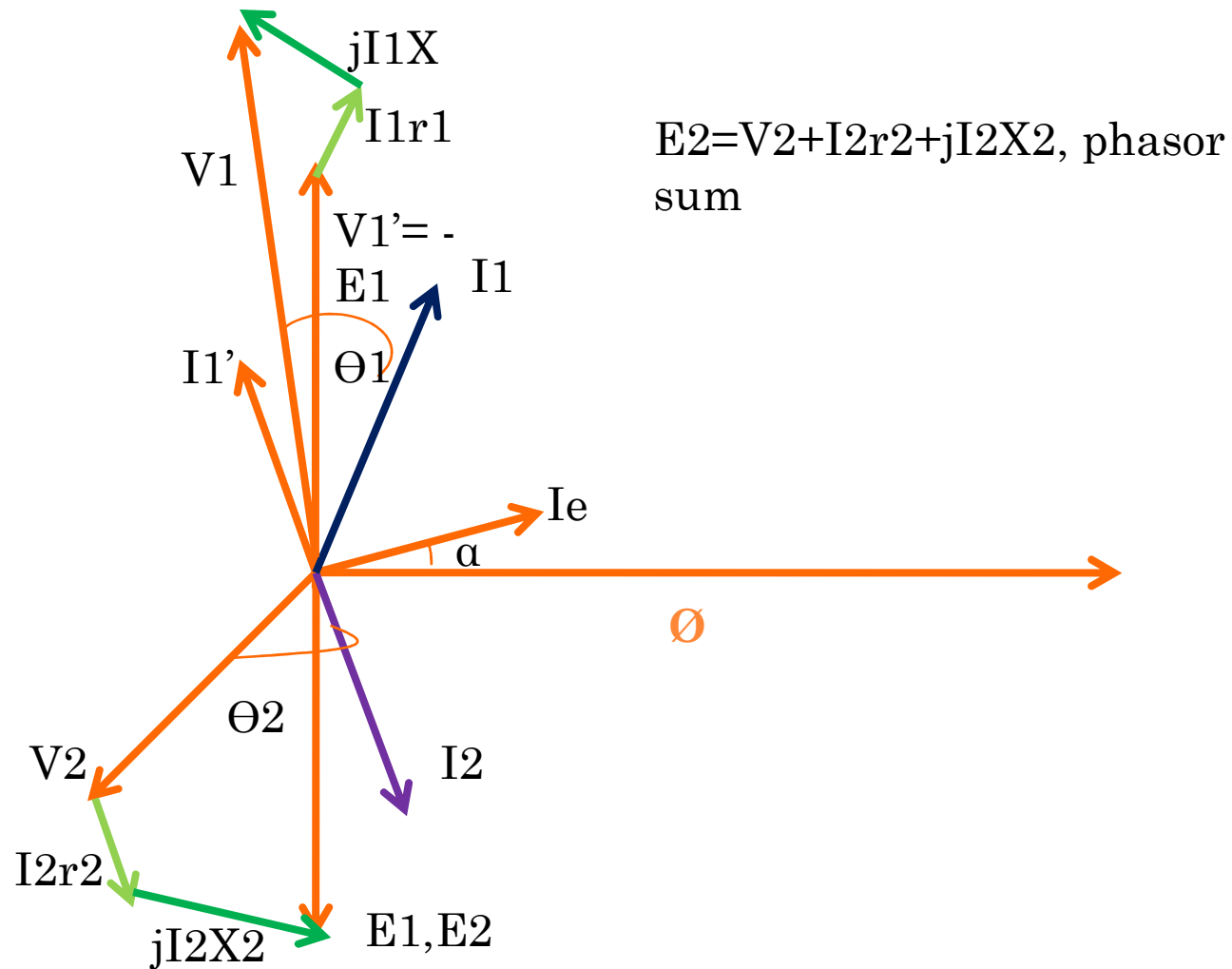PHASOR OF A TRANSFORMER FOR CAPACITIVE LOAD



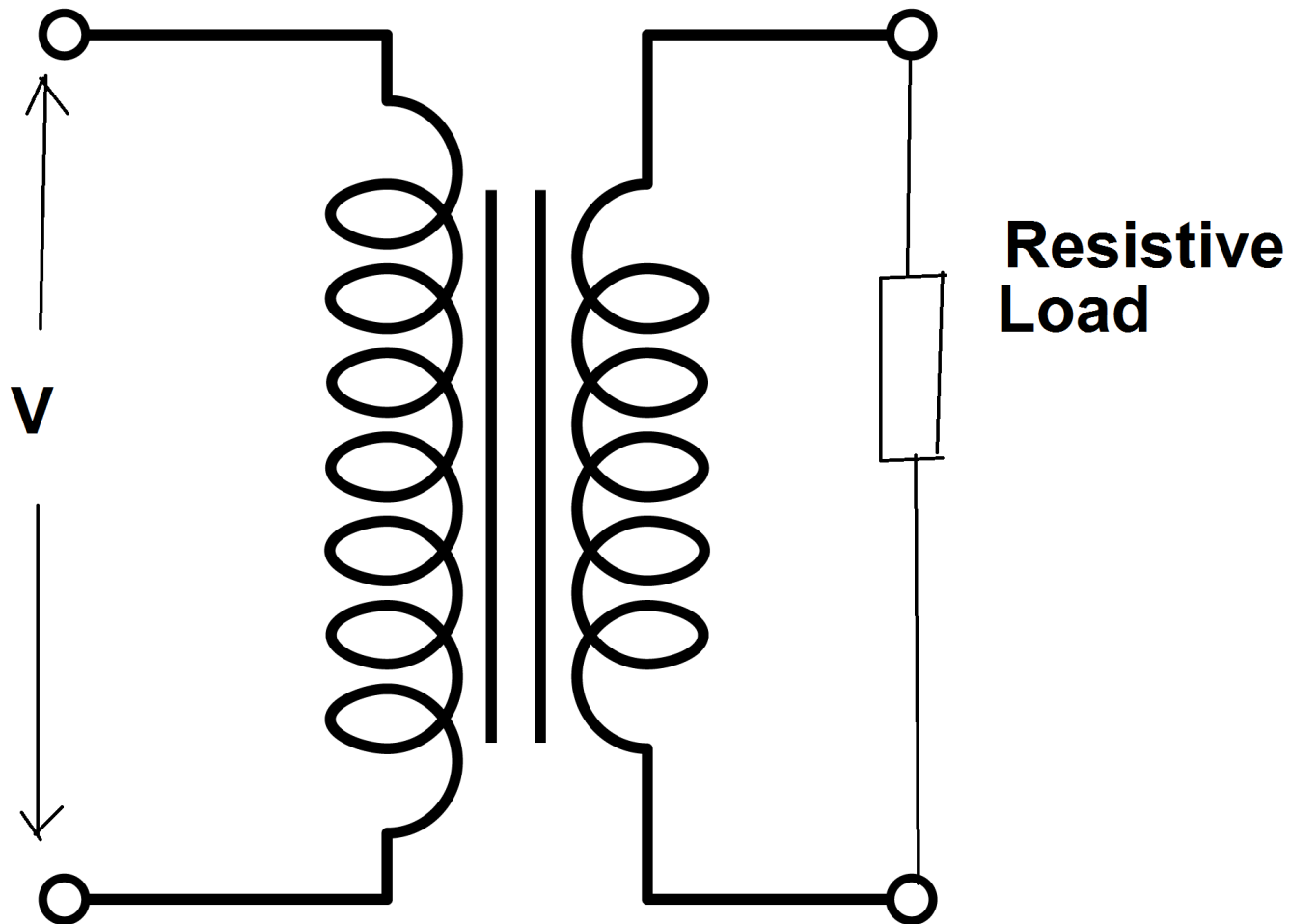PHASOR OF A TRANSFORMER FOR RESISTIVE LOAD



PHASOR OF A TRANSFORMER FOR RESISTIVE LOAD

- For Resistive Load, load current will be in phase with the load Voltage V_2 .



PHASOR OF A TRANSFORMER FOR RESISTIVE LOAD


- Working Flux Φ is taken as reference.




PHASOR OF A TRANSFORMER FOR RESISTIVE LOAD



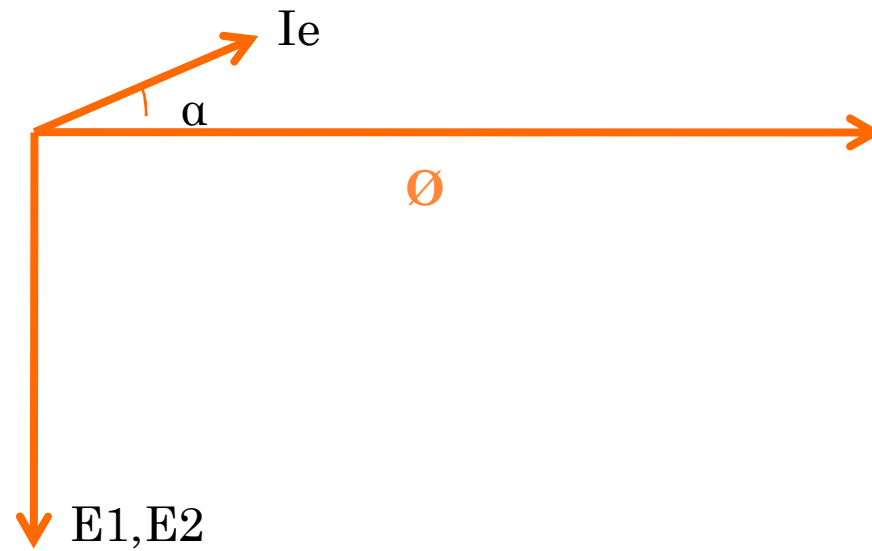
PHASOR OF A TRANSFORMER FOR RESISTIVE LOAD



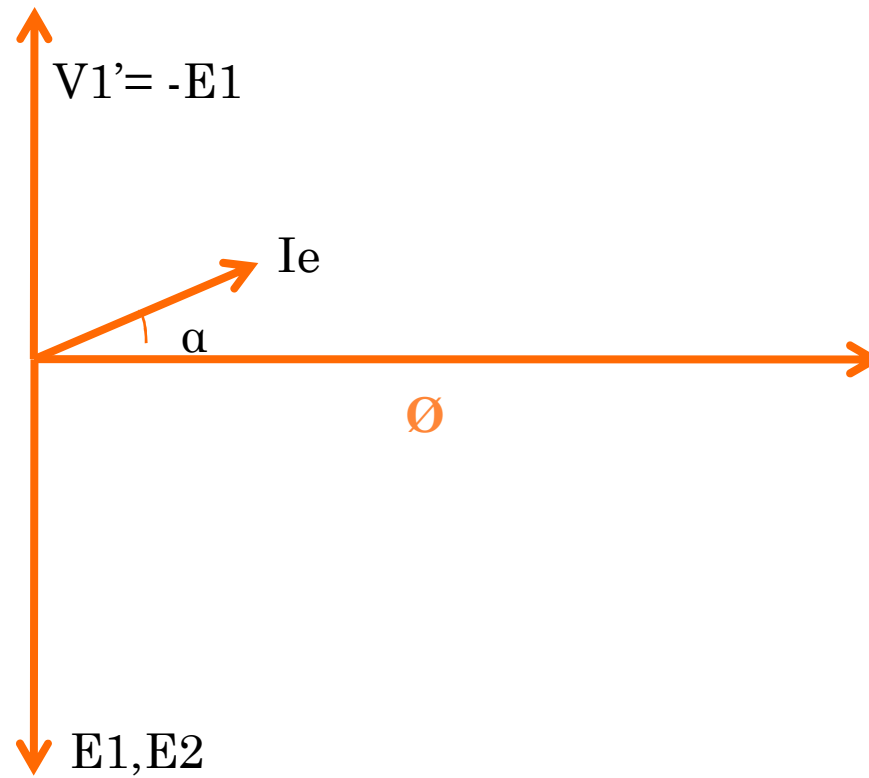
PHASOR OF A TRANSFORMER FOR RESISTIVE LOAD



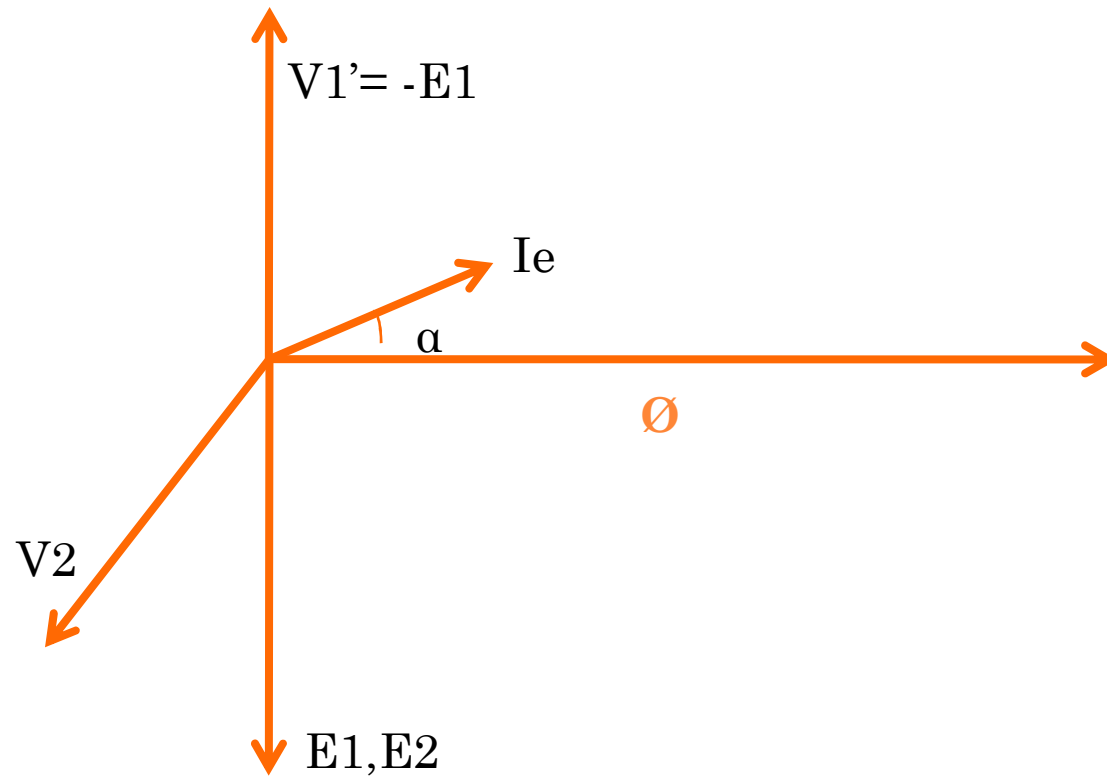
PHASOR OF A TRANSFORMER FOR RESISTIVE LOAD



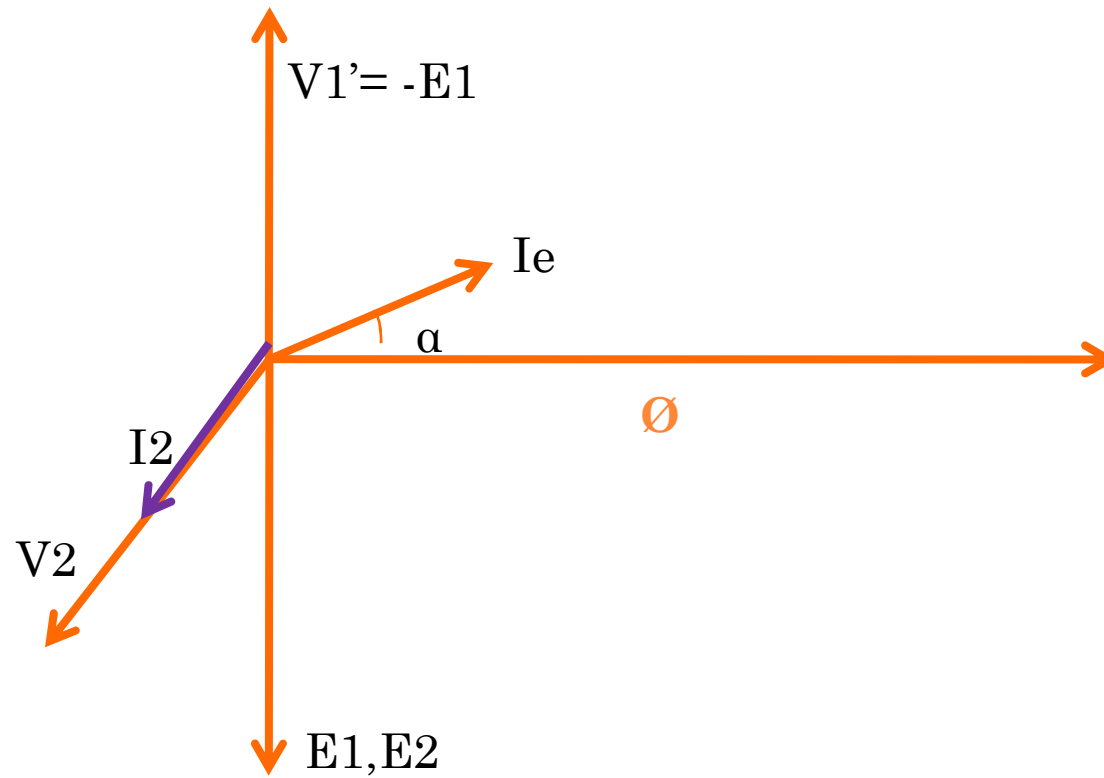
PHASOR OF A TRANSFORMER FOR RESISTIVE LOAD



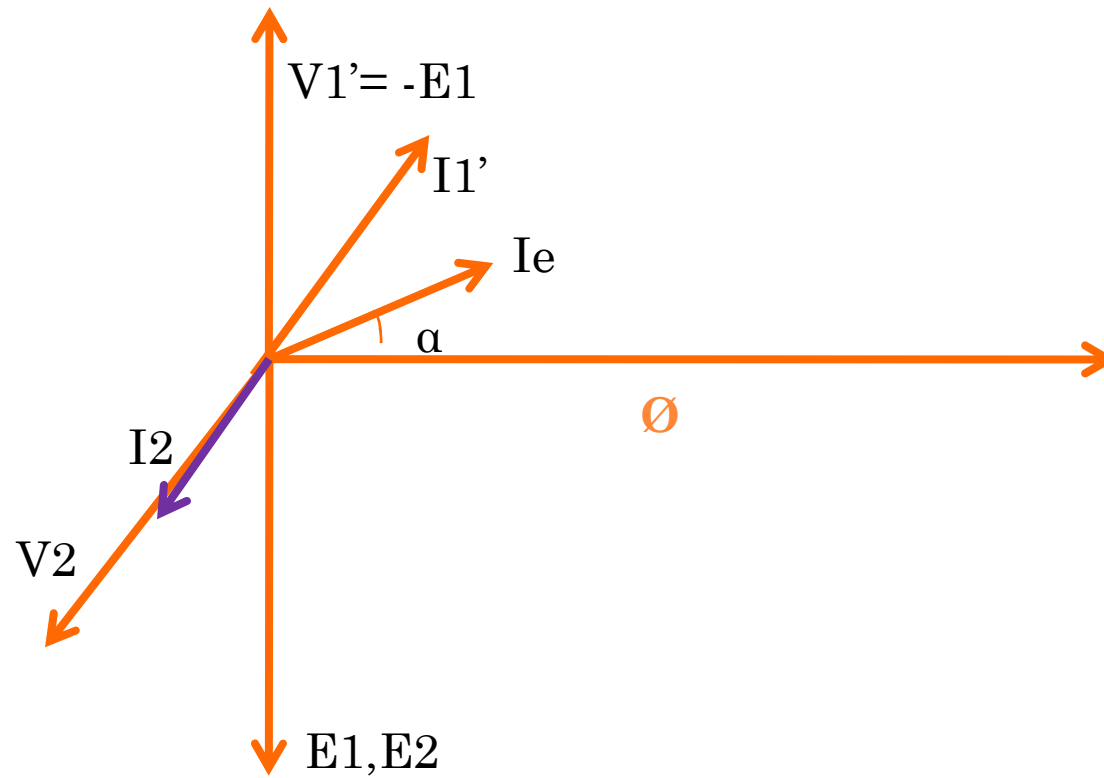
PHASOR OF A TRANSFORMER FOR RESISTIVE LOAD



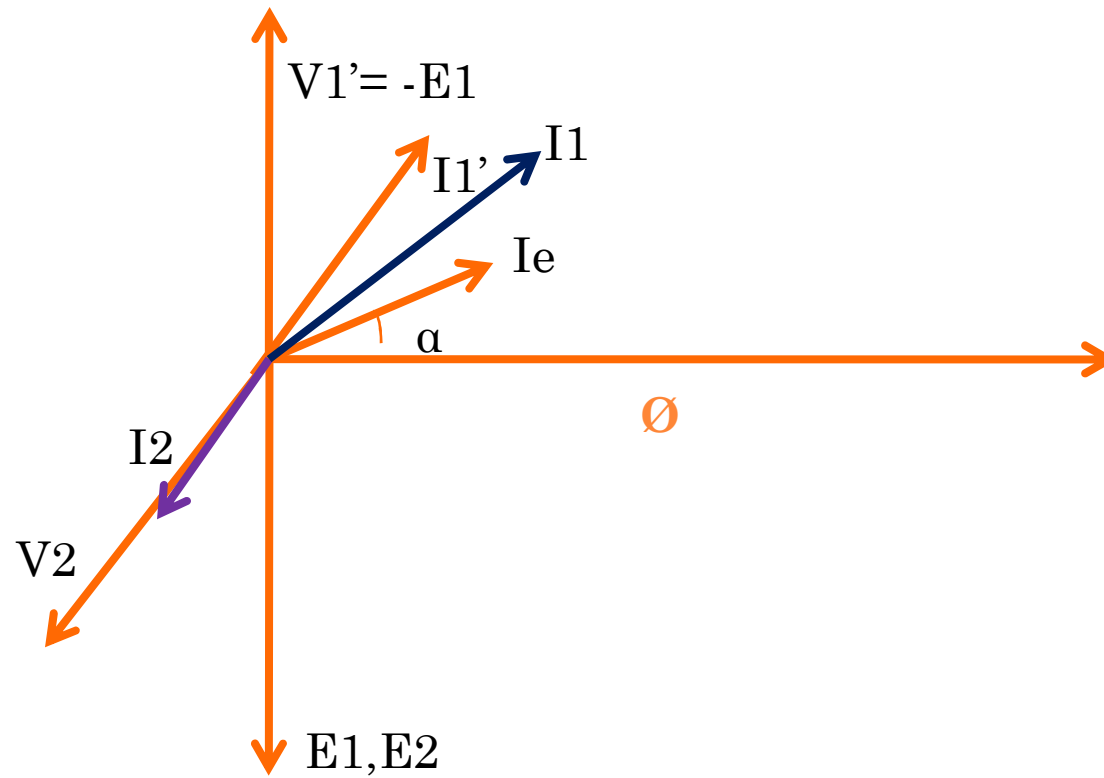
PHASOR OF A TRANSFORMER FOR RESISTIVE LOAD



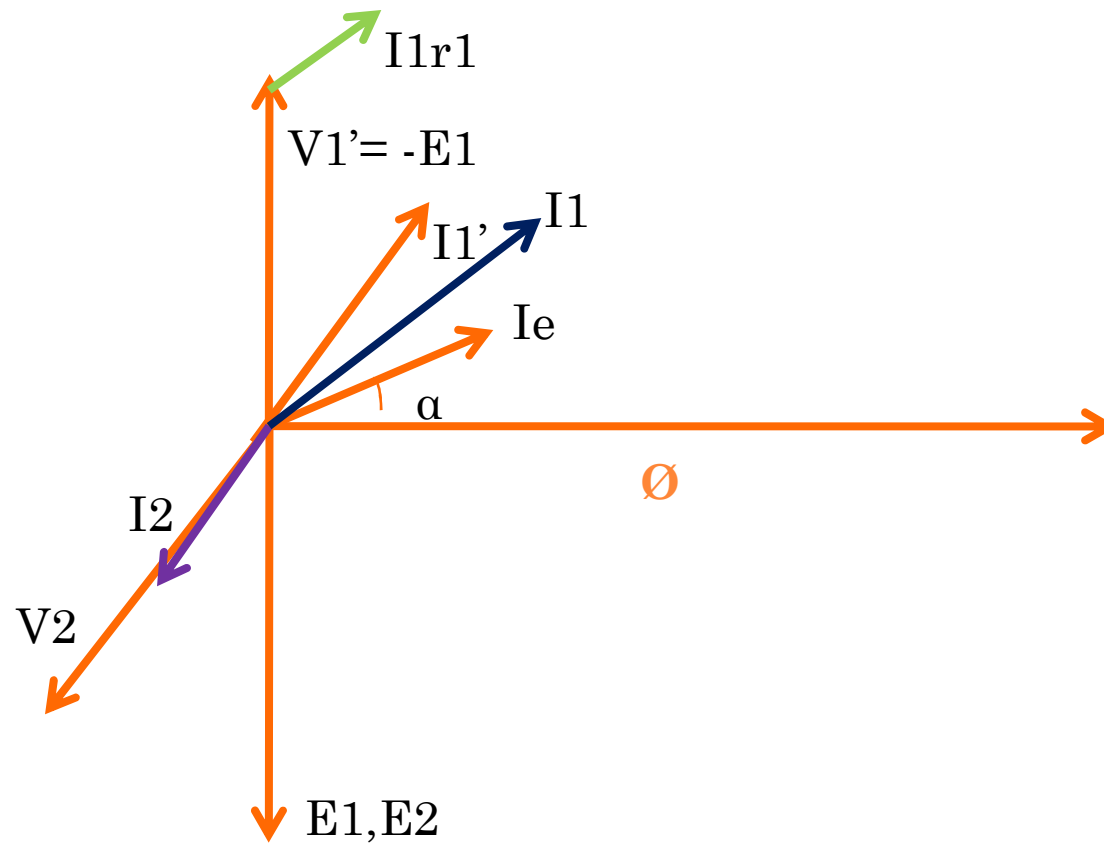
PHASOR OF A TRANSFORMER FOR RESISTIVE LOAD



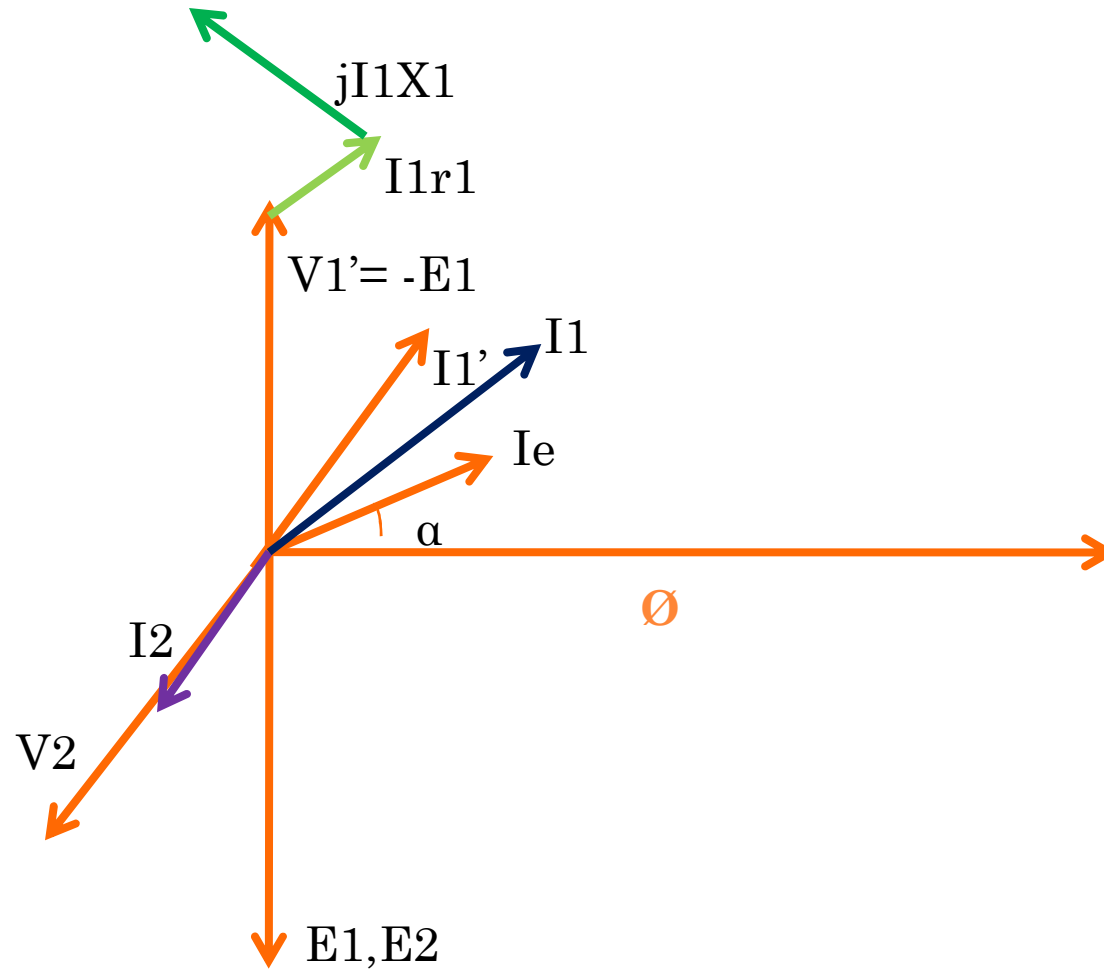
PHASOR OF A TRANSFORMER FOR RESISTIVE LOAD



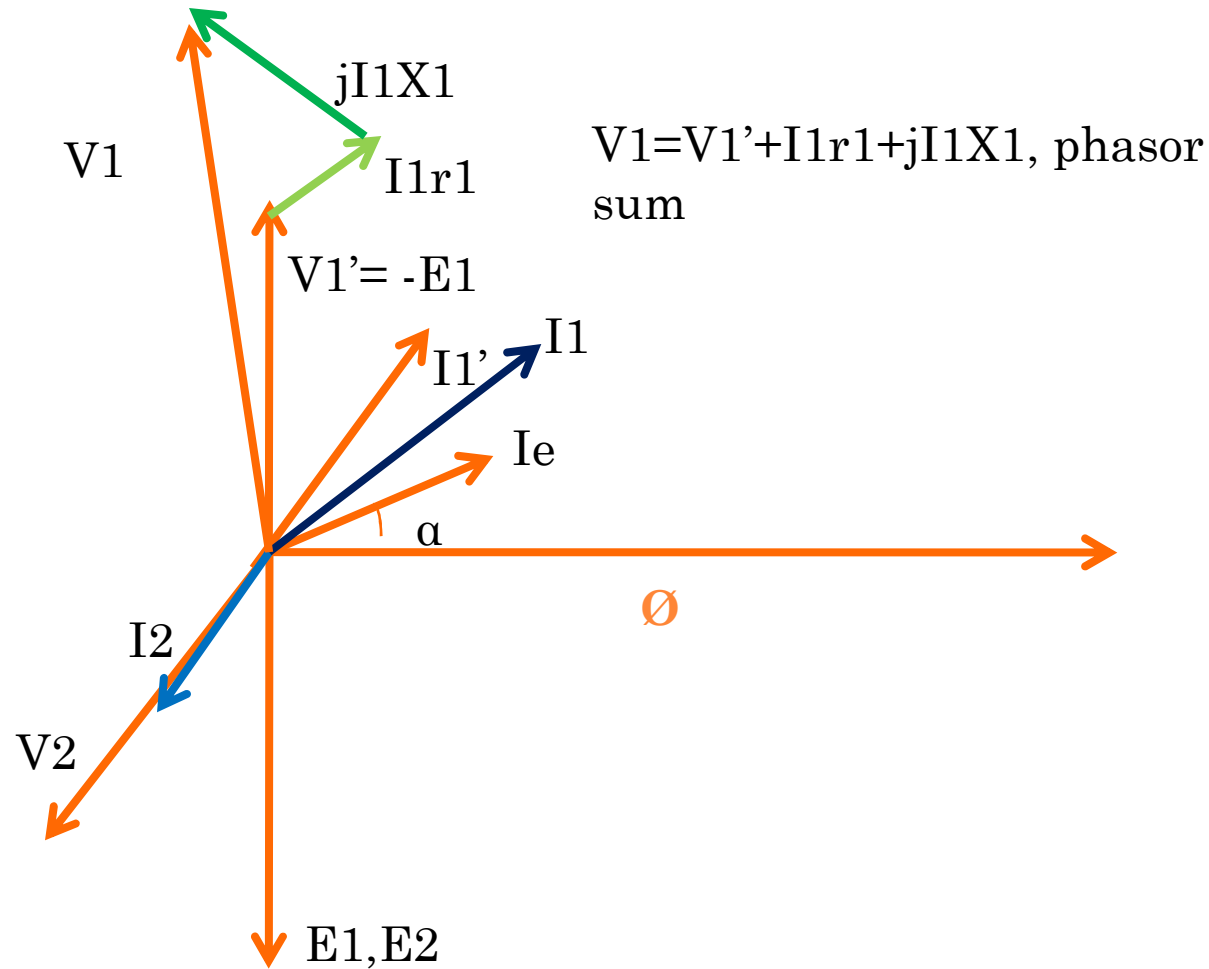
PHASOR OF A TRANSFORMER FOR RESISTIVE LOAD



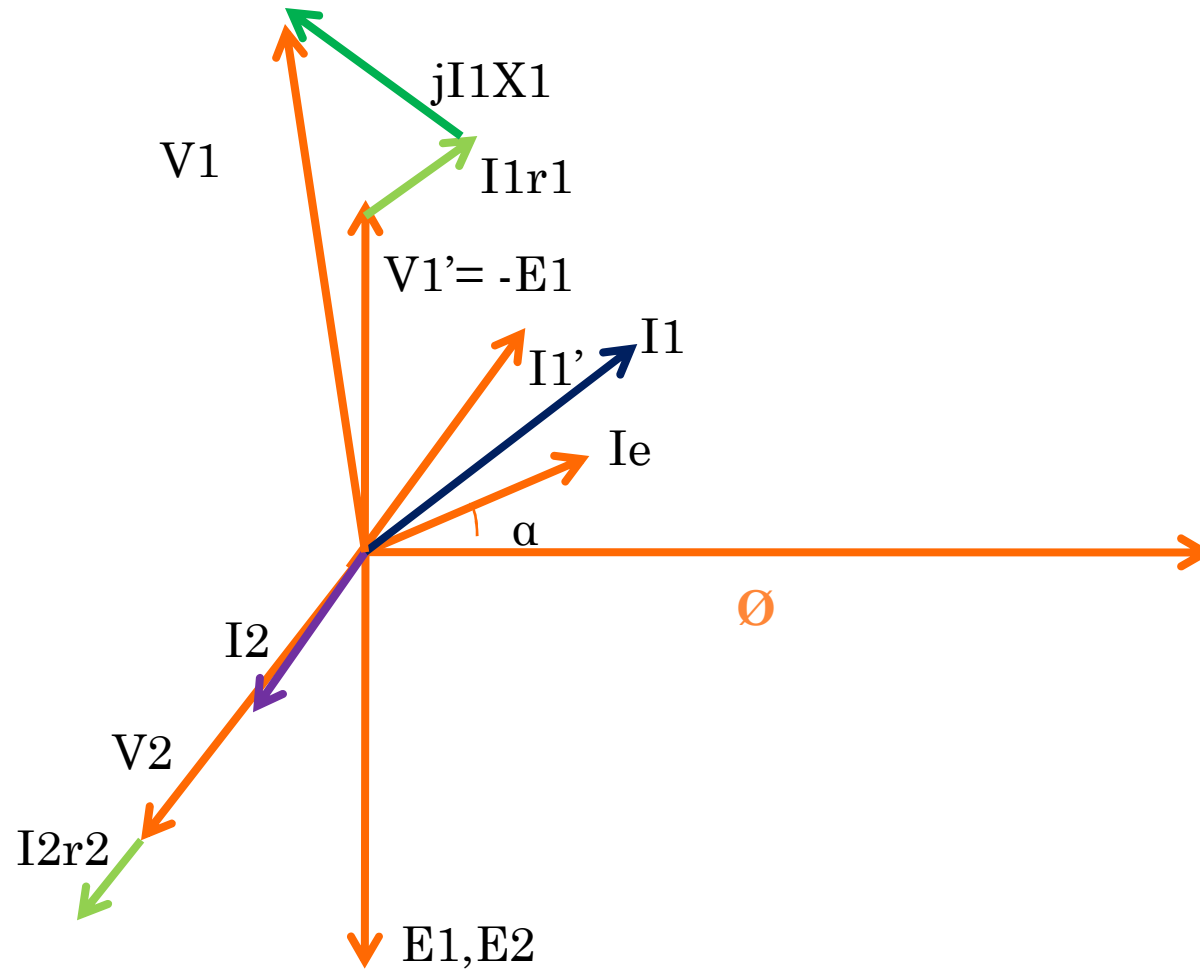PHASOR OF A TRANSFORMER FOR RESISTIVE LOAD



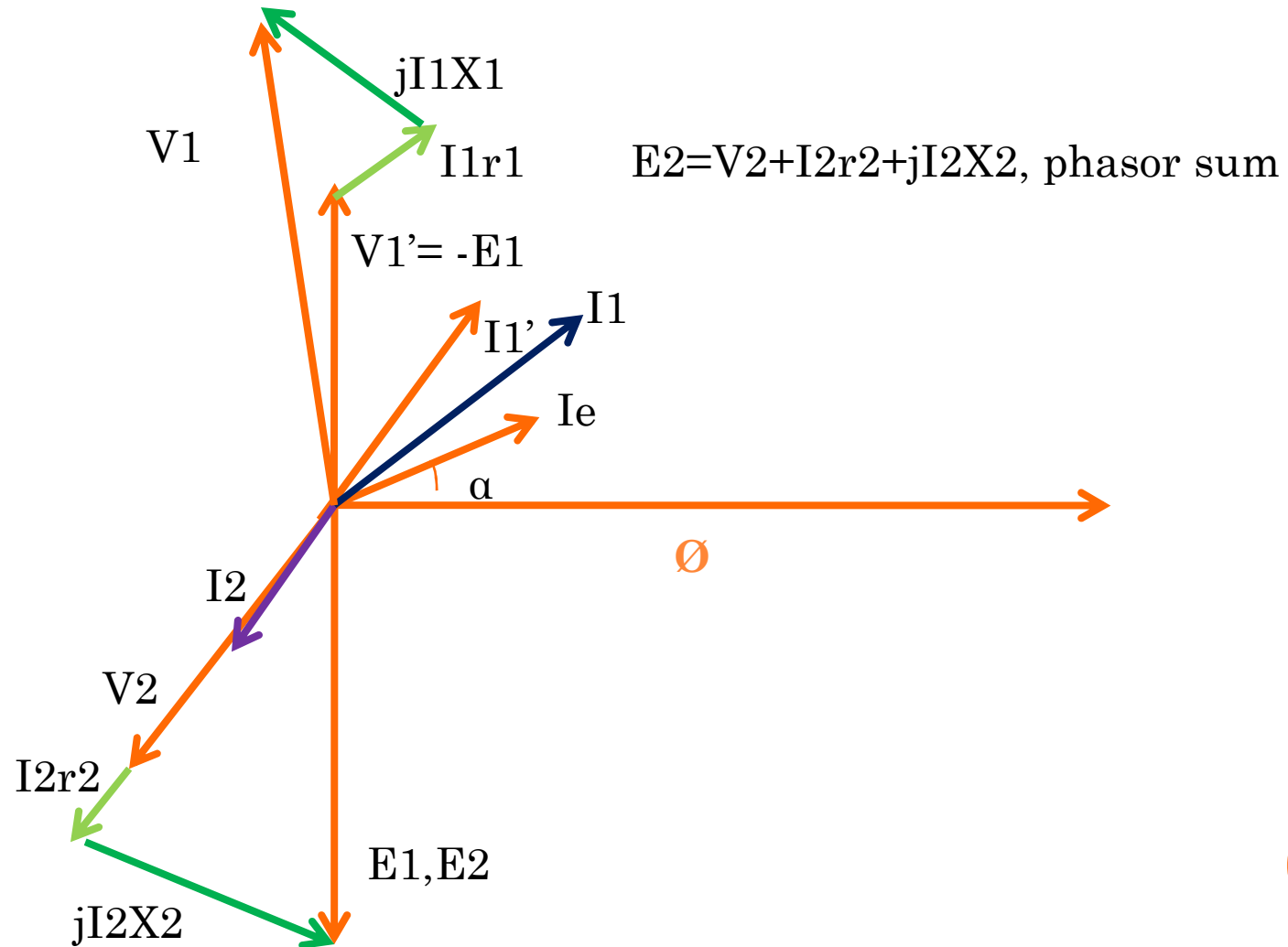PHASOR OF A TRANSFORMER FOR RESISTIVE LOAD



COMMENTS? / QUESTIONS???

